
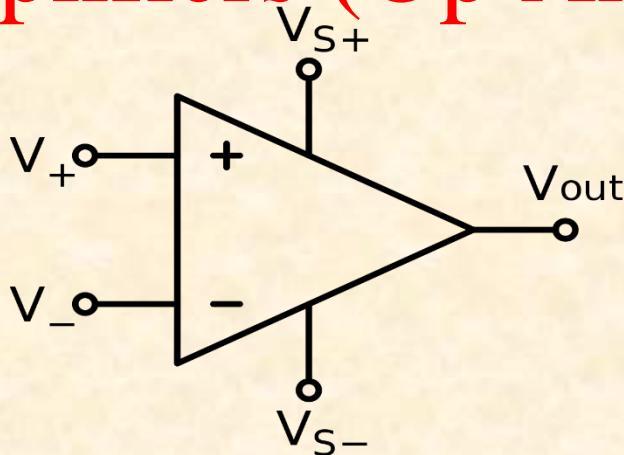


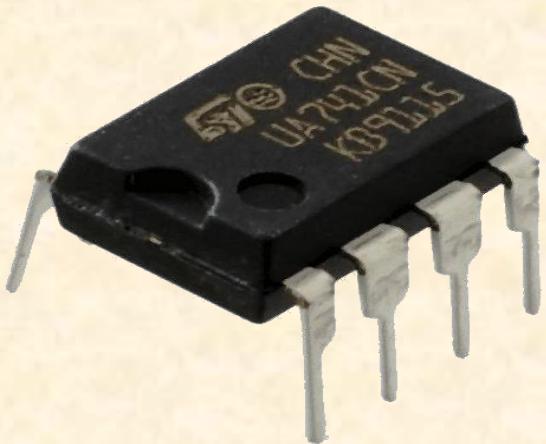

Second stage : Power electronics



Operational Amplifiers (Op Amps)



Abdul ghafor Abdul Ghafar
Abdul hameed

Outline

- The Differentiator
- Example
- The Integrator
- Example
- The Differential Op-amp
- OP-AMP Voltage follower

The Differentiator

The Differentiator:- it is one of inverting op-amp applications as shown in figure bellow.


$$V_o = I_f R_f \quad (1)$$

$$I_f = -I_1 \quad (2)$$

$$I_1 = C \frac{dV_1}{dt} \quad (3)$$


Therefore:-
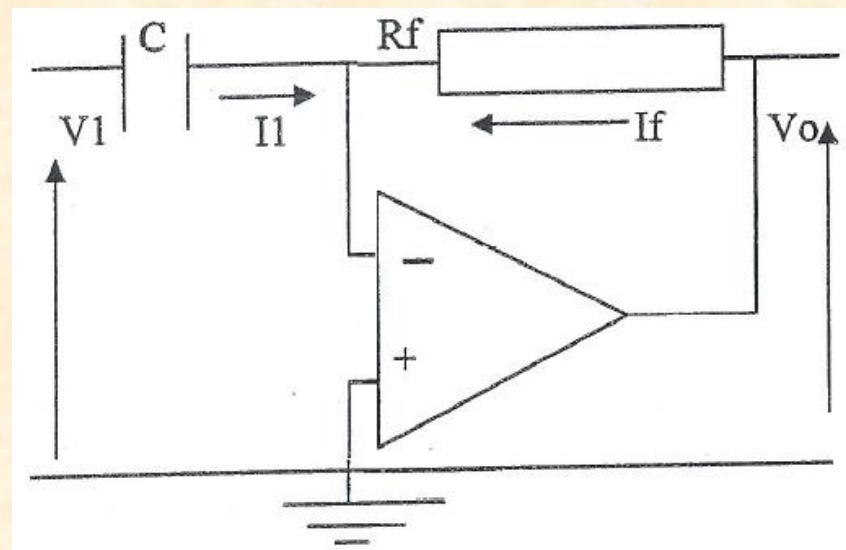
$$V_o = -R_f C \frac{dV_1}{dt} \quad (4)$$



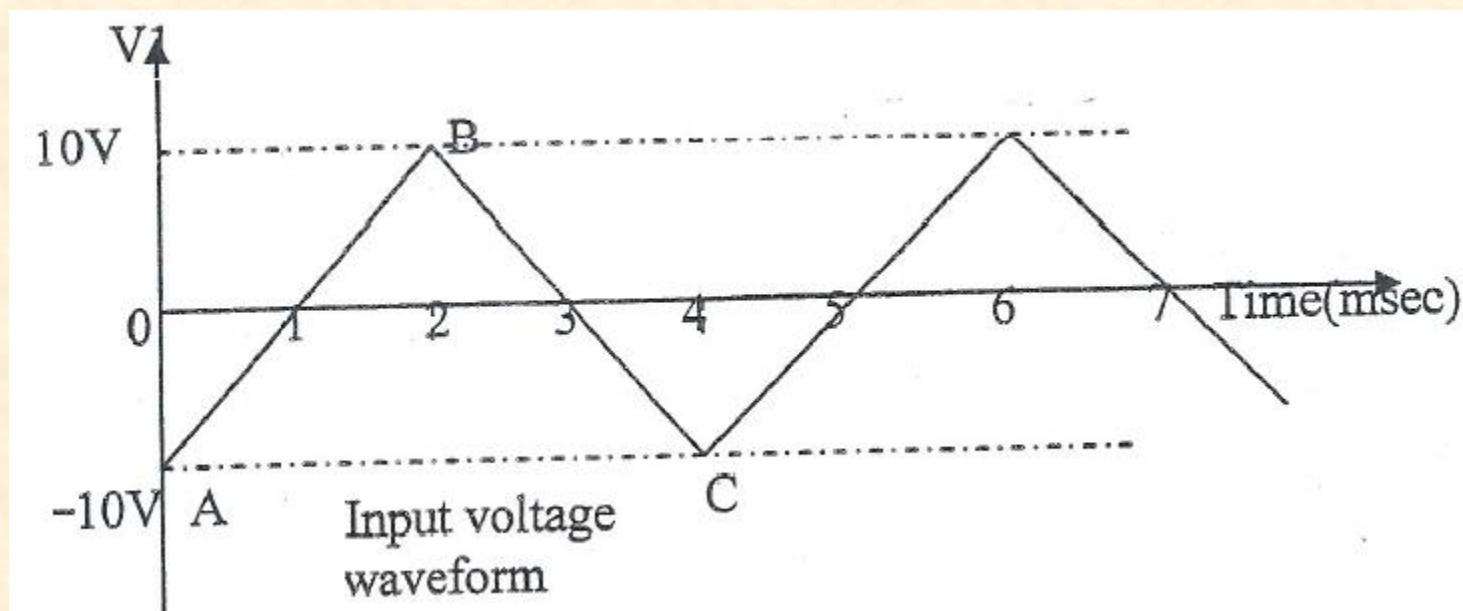Example

For the differentiator shown in figure above; if $R_f = 10K\Omega$ and the value of the capacitor is $0.001\mu F$, the input signal is given in Figure bellow. Find the output voltage waveform.



Cont.

SOL.

من الشكل نلاحظ ان تغير الإشارة خطيا من A الى B وبقيمة ميل ثابتة تمثل المشتقه وتحسب كما يلي:-

$$\frac{dv_1}{dt} = \frac{+10 - (-10)}{2 \times 10^{-3} - 0} = \frac{20}{2 \times 10^{-3}}$$

$$\frac{dv_1}{dt} = 10^4 v/sec$$

And

$$V_o = -RfC \frac{dv_1}{dt} = -(10^4) \times (0.001 \times 10^6) \times (10^4 V/s) = -0.1V$$

وبنفس الطريقة يحسب الميل لشكل موجة الدخل بين النقاط B و C وكمالي:-

$$\frac{dv_1}{dt} = \frac{-10 - (10)}{4 \times 10^{-3} - 2 \times 10^{-3}} = \frac{-20}{2 \times 10^{-3}}$$


$$\frac{dv_1}{dt} = -10^4 v/sec$$

And

$$V_o = -RfC \frac{dv_1}{dt} = -(10^4) \times (0.001 \times 10^6) \times -(10^4 V/s) = 0.1V$$

Cont.

وبذلك يكون شكل موجة الإخراج كالاتي :-

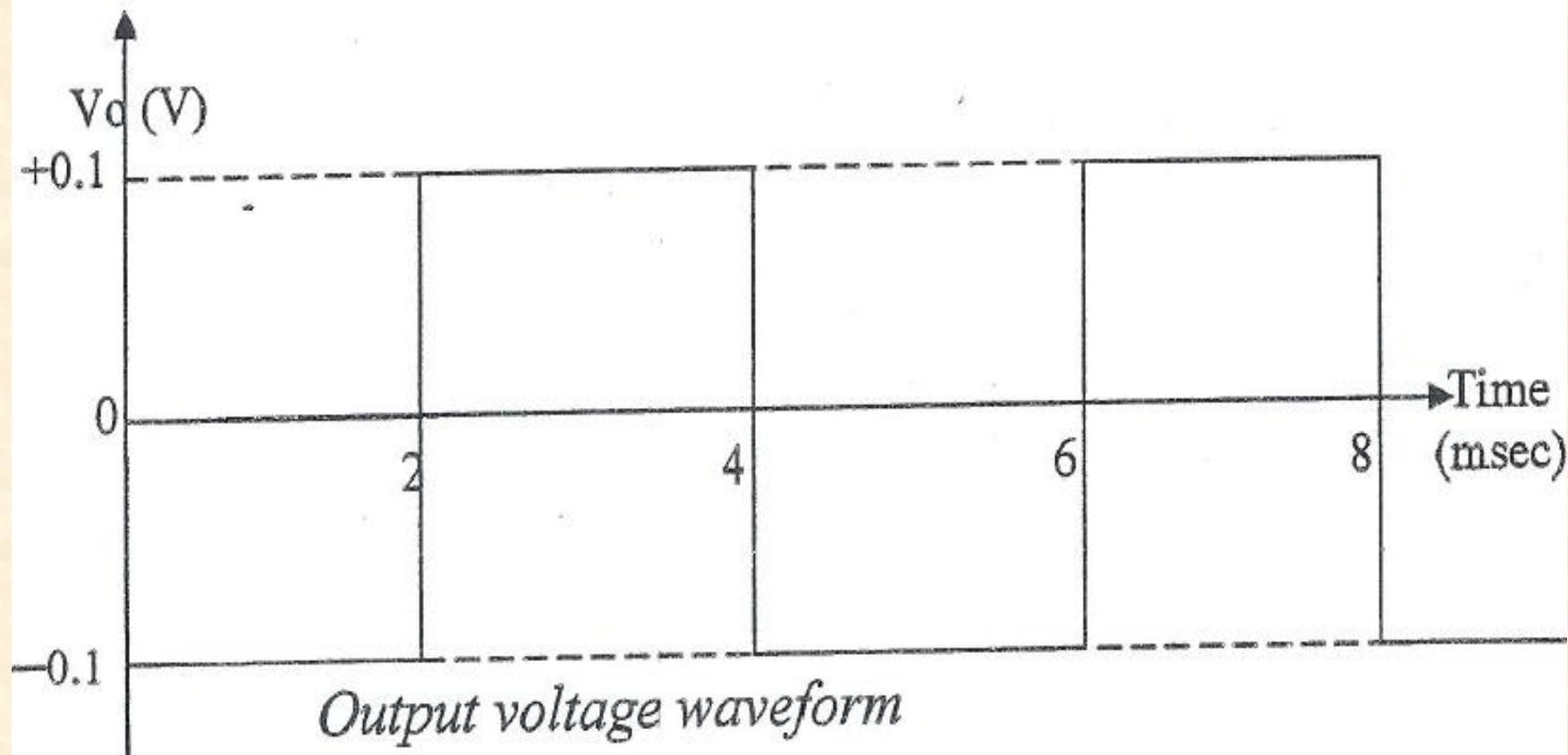

The Integrator

The Integrator:- It is one of the inverting op-amp application as shown in figure bellow.


$$I_f = -I_1 \quad (1)$$

$$I_f = C \frac{dV_o}{dt} \quad (2)$$

$$I_1 = V_1 / R_1 \quad (3)$$

Sub.(2) &(3) into (1)
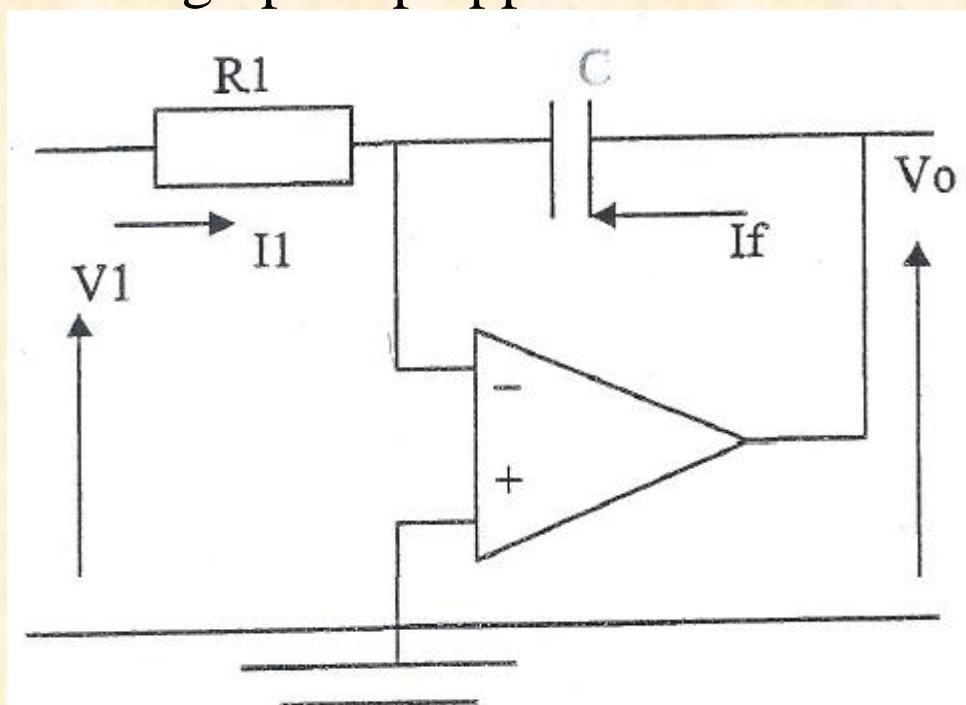
$$C \frac{dV_o}{dt} = -\frac{V_1}{R_1} \quad (4)$$



Integrate both side of eq.4 and solve yields:-

$$V_o = -\frac{1}{R_1 C} \int V_1 dt \quad (5)$$

Example

The circuit shown in Figure bellow:- show that the output E_o is given as

$$E_o = \frac{2}{Rc} \int E_i dt$$


SOL.

$$V_1 = V_2 \quad (1)$$

$$V_1 = [R/(R+R)]E_o = \frac{1}{2}E_o \quad (2)$$

$$I_1 + I_2 = I_3 \quad (3)$$
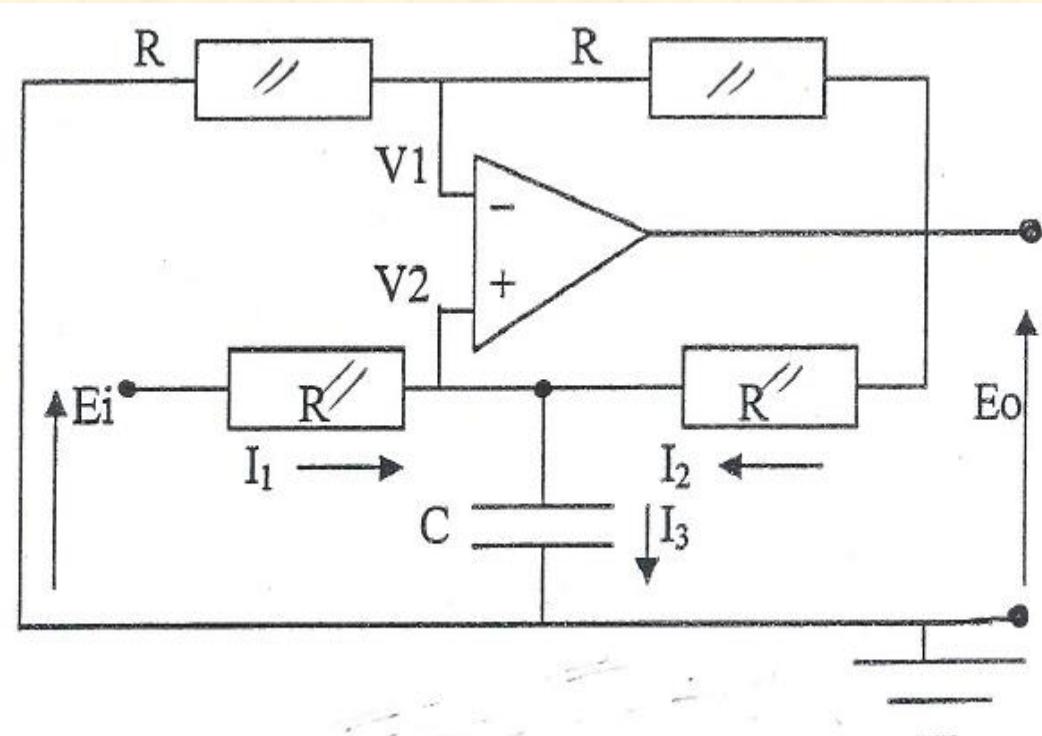
$$\frac{E_i - V_1}{R} + \frac{E_o - V_1}{R} = C \frac{dV_1}{dt} \quad (3)$$




$$\frac{E_i - (\frac{1}{2})E_o}{R} + \frac{E_o - (\frac{1}{2})E_o}{R} = C \frac{d(\frac{1}{2})E_o}{dt}$$

$$E_o = \frac{2}{RC} \int E_i dt$$

The Differential Op-amp

The Differential Op-amp

$$V_o = [V_2 - V_1] \frac{R_f}{R_1}$$

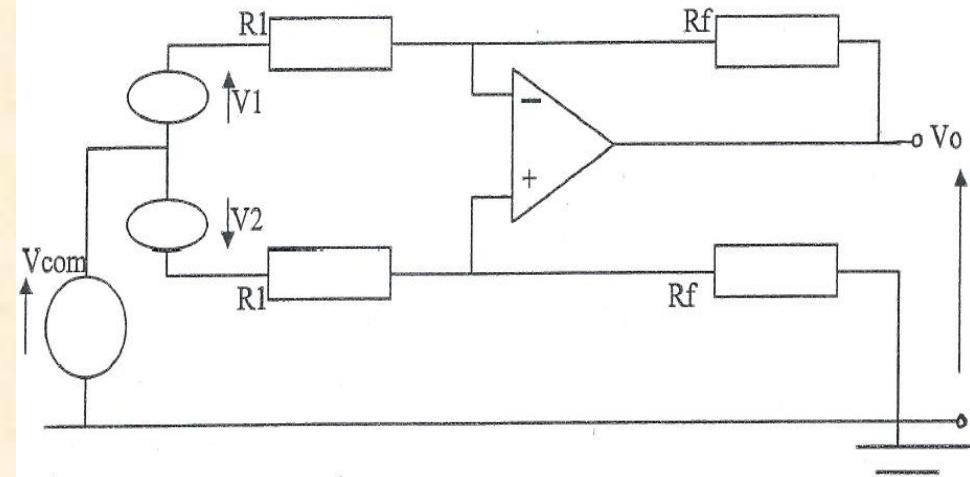

OP-AMP Voltage follower

OP-AMP Voltage follower

$$V_o = V_1$$

