

Node and supernode analysis's

procedure !

- (1) Select a node as the reference node
- (2) Assign voltages v_1, v_2, \dots to the remaining nodes, The voltages are referenced with respect to the reference node
- (3) Apply KCL to each node except the reference node
- (4) Use Ohm's Law to express the branch currents in terms of the node voltages
- (5) Solve the resulting simultaneous equations to obtain the unknown node voltages

We usually take the ground node as the reference node with $V=0$

$$\bar{V} = 0$$

Examples

Example 1: single node

KCL at node (1)


$$i_1 + i_2 + i_3 = 0 \quad \text{--- (1)}$$

$$i_1 = \frac{V_1 - 20}{5}$$

$$i_2 = \frac{V_1}{10}$$

$$i_3 = \frac{V_1 - 8}{2}$$

} --- (2)

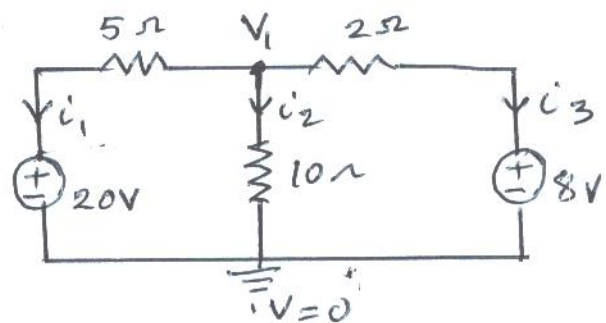

using (2) in (1):

$$\frac{V_1 - 20}{5} + \frac{V_1}{10} + \frac{V_1 - 8}{2} = 0$$


$$V_1 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} \right) = \frac{20}{5} + \frac{8}{2} \quad \text{4+4+5}$$

$$V_1 \left(\frac{2+1+5}{10} \right) = 8$$

$$\underline{V_1 = 10 \text{ V}}$$

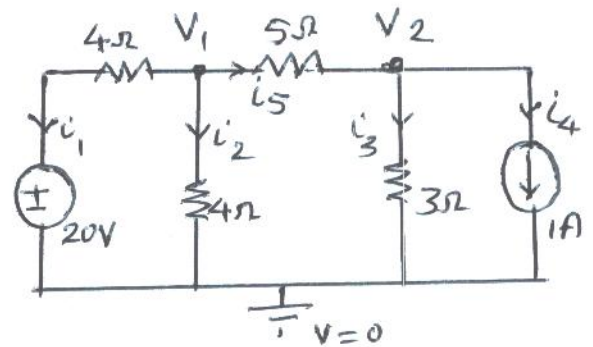Example 2 : 2 nodes

Using nodal analysis, find V_1 and V_2 at nodes indicated (1) and (2) in the circuit shown in the Figure



Solution :

KCL at node 1

$$i_1 + i_2 + i_5 = 0 \quad \text{--- (1)}$$

$$i_1 = \frac{V_1 - 20}{4}, \quad i_2 = \frac{V_1}{4}, \quad i_5 = \frac{V_1 - V_2}{5} \quad \text{--- (2)}$$

Sub (2) in (1) :

$$\frac{V_1 - 20}{4} + \frac{V_1}{4} + \frac{V_1 - V_2}{5} = 0$$

$$V_1 \left(\frac{1}{4} + \frac{1}{4} + \frac{1}{5} \right) - \frac{V_2}{5} = 5 \Rightarrow V_1 \left(\frac{1}{2} + \frac{1}{5} \right) - \frac{V_2}{5} = 5$$

$$\frac{7V_1}{10} - \frac{V_2}{5} = 5$$

$$\underline{7V_1 - 2V_2 = 50} \quad \text{--- (3)}$$

KCL at node 2

$$i_3 + i_4 - i_5 = 0 \quad \text{--- (4)}$$

$i_3 = \frac{V_2}{3}$, $i_4 = 1$ ----- (5)

Using (5) in (4)

$\frac{V_2}{3} + 1 - \frac{V_1 - V_2}{5} = 0$


$-3V_1 + 8V_2 = -15$ ----- (6)

$D = \begin{vmatrix} 7 & -2 \\ -3 & 8 \end{vmatrix} = 56 - 6 = 50$

$V_1 = \frac{1}{50} \begin{vmatrix} 50 & -2 \\ -15 & 8 \end{vmatrix} = \frac{1}{50} (400 - 30) = \frac{37}{5} V$

$V_2 = \frac{1}{50} \begin{vmatrix} 7 & 50 \\ -3 & -15 \end{vmatrix} = \frac{1}{50} (-105 + 150)$
 $= \frac{45}{50} = 0.9 V$

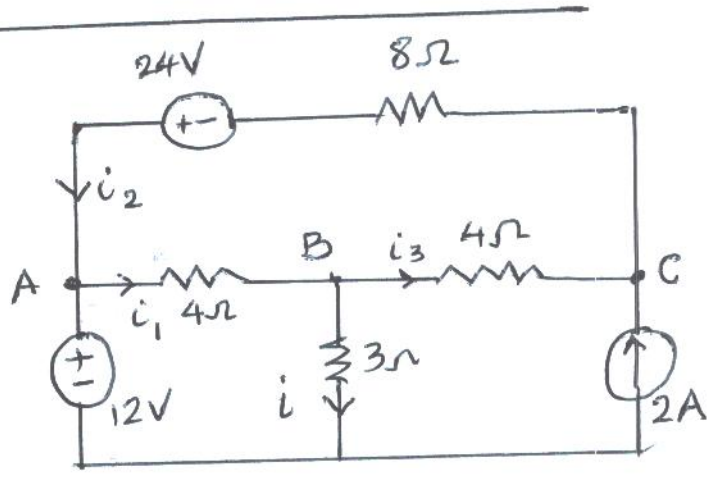Example 3 : 3 nodes
Find nodal voltages V_A, V_B and V_C in the circuit shown in the Figure.



Solution :

$V_A = 12 V$

$i_1 = \frac{V_A - V_B}{4} = \frac{12 - V_B}{4}$ ----- (1)

$i_2 = \frac{V_C + 24 - V_A}{8} = \frac{V_C - 36}{8}$ ----- (2)

$i = \frac{V_B}{3}$, $i_3 = \frac{V_B - V_C}{4}$ ----- (3)

KCL at B

$$i_1 = i_3 + i$$

$$\frac{12 - V_B}{4} = \frac{V_B - V_C}{4} + \frac{V_B}{3}$$

$$\frac{5}{6} V_B - \frac{1}{4} V_C = 3 \quad \text{--- (4)}$$

KCL at C :

$$2 = i_3 + i_2$$

$$2 = \frac{V_B - V_C}{4} + \frac{V_C - 36}{8}$$

Simplify :

$$2V_B - V_C = -20 \quad ** \quad \text{--- (5)}$$

$$V_A + 0V_B + 0V_C = 12 \quad * \quad \text{--- (6)}$$

$$10V_B - 3V_C = 36 \quad ** * \quad \text{--- (4)}$$

$$D = \begin{vmatrix} 1 & 0 & 0 \\ 0 & 2 & -1 \\ 10 & -10 & -3 \end{vmatrix} = -6 + 10 = 4$$

$$V_A = \frac{1}{4} \begin{vmatrix} +12 & 0 & 0 \\ -20 & 2 & -1 \\ 36 & 10 & -3 \end{vmatrix} = \frac{1}{4} (+120) (-6 + 10) = +120$$

$$V_B = \frac{1}{4} \begin{vmatrix} 1 & +12 & 0 \\ 0 & -20 & -1 \\ 0 & 36 & -3 \end{vmatrix} = \frac{1}{4} (+60 + 36) - 12 \times 0$$

$$= \frac{1}{4} (96) = 24 \text{ V}$$


$$V_C = \frac{1}{4} \begin{vmatrix} 1 & 0 & 12 \\ 0 & 2 & -20 \\ 0 & 10 & 36 \end{vmatrix} = \frac{72 + 200}{4} = \frac{272}{4} = 68 \text{ V}$$

Home work

(5)

Prob. 1 :


Find I_0 in the circuit shown in the Fig using nodal analysis. (Ans: $I_0 = \frac{3}{4} A$)

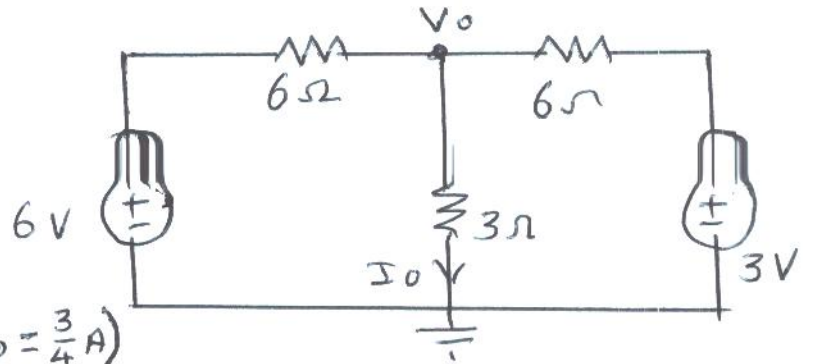

Prob. 2 :

Find V_1 and V_2 using nodal analysis


(Ans: $V_1 \approx 2.6V, V_2 \approx 29V$)

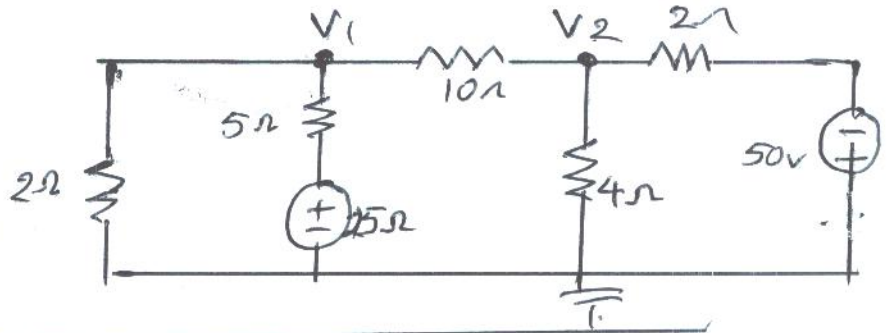

Prob. 3 :

Find V_1, V_2 and V_3 in the Fig.


(Ans: $V_1 = 80V, V_2 \approx -64V, V_3 \approx 156V$)

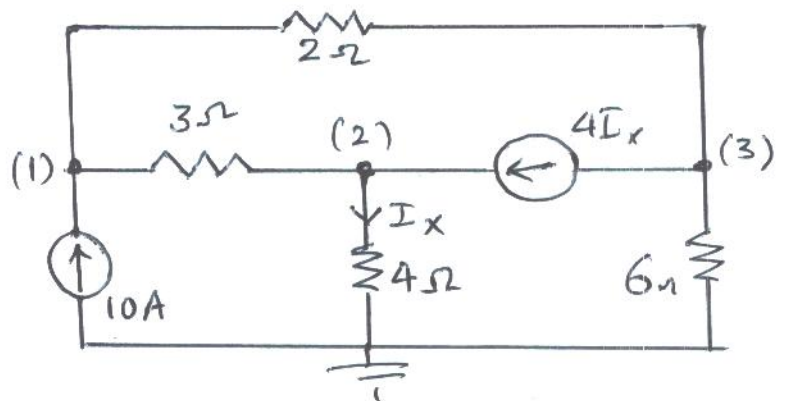

Prob 4 :


Find V_1 and V_2 using nodal analysis

(Ans: $V_1 = 3.38V, V_2 = -5V$)

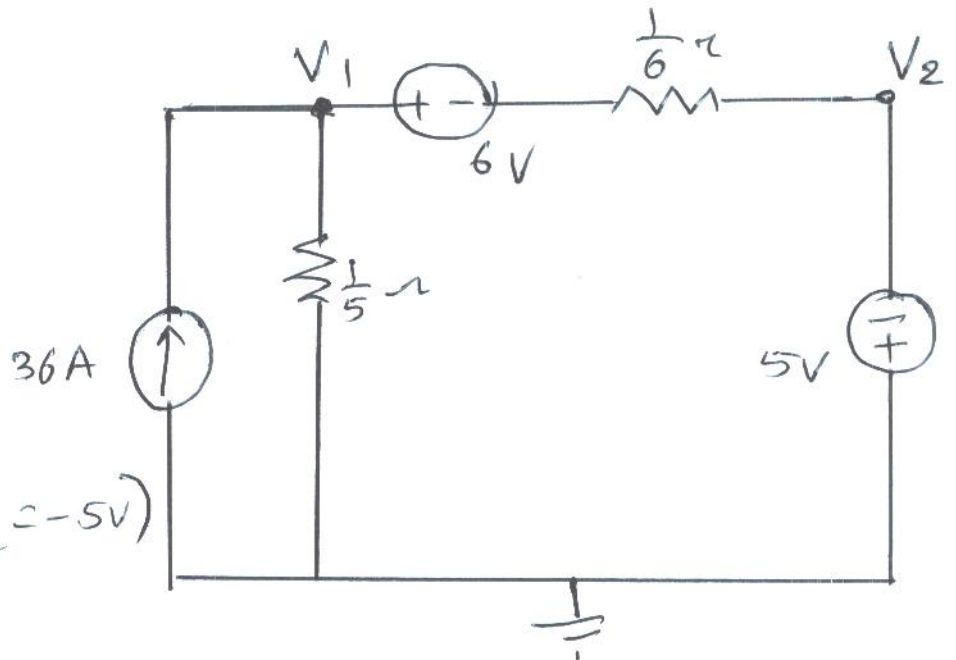

Supernode analysis

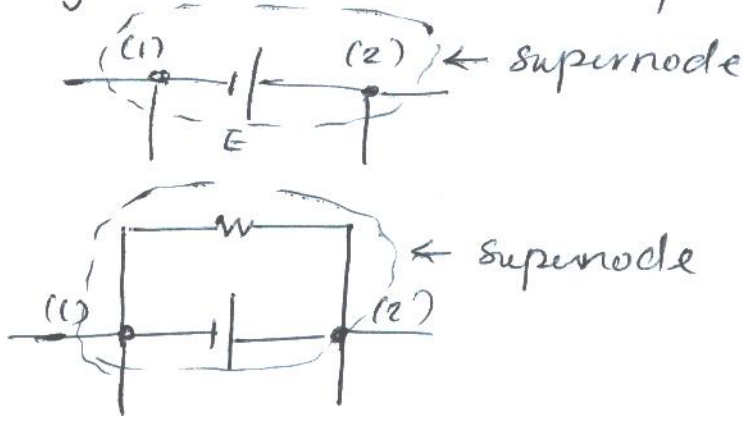
A supernode is formed by enclosing a voltage source connected between two nonreference nodes and any elements connected in parallel with it



Examples

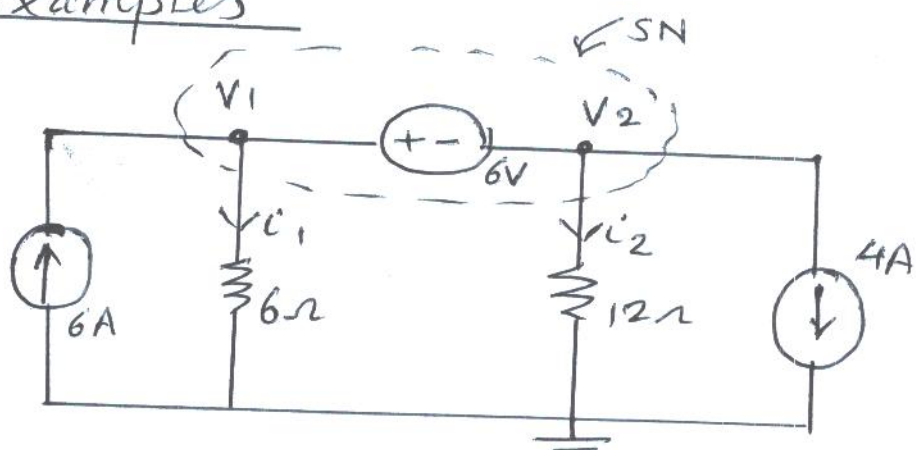Example 1:

Determine V_1 and V_2 in the circuit shown in the Figure



Solution:

KCL for SN : $\sum_{SN} i = 0$

$$i_1 + i_2 - 6 + 4 = 0$$

$$i_1 + i_2 = 2 \quad \text{--- (1)}$$

$$i_1 = \frac{V_1}{6}, \quad i_2 = \frac{V_2}{12} \quad \text{--- (2)}$$

using (2) in (1)

$$\frac{V_1}{6} + \frac{V_2}{12} = 2$$

$$2V_1 + V_2 = 24 \quad \text{--- (3)}$$

Inside SN : $V_1 - V_2 = 6 \quad \text{--- (4)}$

solve (3) and (4)


$$D = \begin{vmatrix} 2 & 1 \\ 1 & -1 \end{vmatrix} = -3$$

$$V_1 = \frac{\begin{vmatrix} 24 & 1 \\ 6 & -1 \end{vmatrix}}{D} = -\frac{1}{3} [-24 - 6] = 10V$$

$$V_2 = -\frac{1}{3} \begin{vmatrix} 2 & 24 \\ 1 & 6 \end{vmatrix} = -\frac{1}{3} (12 - 24) = 4V$$

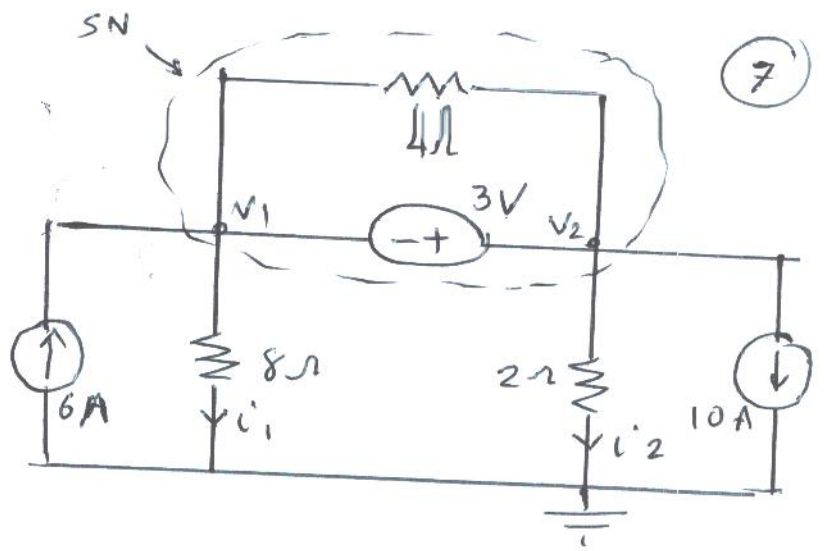Example 2

Determine V_1 and V_2 in the circuit shown in the Fig using the concept of a supernode



Solution

apply KCL on SN

$$\sum_{SN} i = 0$$

$$6 = i_1 + i_2 + 10$$

$$\therefore i_1 + i_2 = -4 \quad \text{--- (1)}$$

$$i_1 = \frac{V_1}{8}, \quad i_2 = \frac{V_2}{2} \quad \text{--- (2)}$$

Using (2) in (1):

$$\frac{V_1}{8} + \frac{V_2}{2} = -4 \quad \text{--- (3)}$$

$$\therefore V_1 + 4V_2 = -32 \quad \text{--- (3)}$$

Inside SN:

$$V_2 - V_1 = 3 \quad \text{--- (4)}$$

$$D = \begin{vmatrix} 1 & 4 \\ -1 & 1 \end{vmatrix} = +5$$

$$V_1 = \begin{vmatrix} -32 & 4 \\ 3 & 1 \end{vmatrix} \left(\frac{1}{+5} \right) = +\frac{1}{5} (-32 - 12) = -\frac{44}{5} \text{ V}$$

$$V_1 = -8.8 \text{ V}$$

$$V_2 = \begin{vmatrix} 1 & -32 \\ -1 & 3 \end{vmatrix} \left(\frac{1}{5} \right) = \frac{1}{5} (3 - 32) = -\frac{29}{5} = -5.8 \text{ V}$$

$$\therefore i_1 = \frac{V_1}{8} = -1.1 \text{ A} \quad \& \quad i_2 = \frac{V_2}{2} = -2.9 \text{ A}$$

Example 3

Determine V_1 and V_2 in the circuit shown in the Figure

Solution :

Current entering SN
= Current leaving SN

$$24 + 7V_2 + 2V_1 = 20$$

$$\therefore 2V_1 + 7V_2 = -4 \quad \text{--- (1)}$$

KCL at node 1 :

$$20 - i_1 + 18 + i = 0$$

$$38 - 2V_1 + 4(V_1 - V_2) = 0$$

$$38 = 6V_1 - 4V_2$$


$$3V_1 - 2V_2 = 19 \quad \text{--- (2)}$$

$$D = \begin{vmatrix} 2 & 7 \\ 3 & -2 \end{vmatrix} = -4 - 21 = -25$$

$$V_1 = \frac{\begin{vmatrix} -4 & 7 \\ 19 & -2 \end{vmatrix}}{D} = \frac{(8 - 133)}{-25}$$

$$= -\frac{1}{25}(-125) = 5V$$

$$V_2 = \frac{\begin{vmatrix} 2 & -4 \\ 3 & 19 \end{vmatrix}}{D} = \frac{-1}{25}(38 + 12) = \frac{-50}{25} = -2V$$

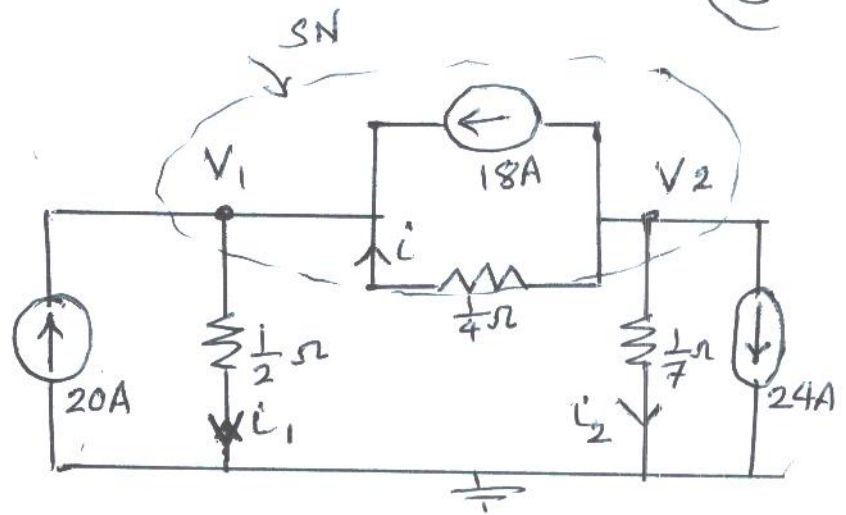

Example 4

Find V_0 using nodal analysis

Solution:

Apply KCL on SN

$$-8 + i_1 + i_2 + i_3 + 2 = 0$$

$$-8 + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2 - V_3}{2} + 2 = 0$$

Simplify

$$2V_1 + V_2 + 3V_2 - 3V_3 = 36$$

$$2V_1 + 4V_2 - 3V_3 = 36 \quad \text{--- (1)}$$

Inside SN

$$V_2 - V_1 = 12 \quad \text{--- (2)}$$

KCL on node 3

$$\frac{V_2 - V_3}{2} + 2 - \frac{V_3}{1} = 0$$

$$V_2 - 3V_3 + 4 = 0$$

$$V_2 - 3V_3 = -4 \quad \text{--- (3)}$$

collect eqs


$$2V_1 + 4V_2 - 3V_3 = 36$$

$$-V_1 + V_2 + 0V_3 = 12$$

$$0V_1 + V_2 - 3V_3 = -4$$

$$\Rightarrow D = \begin{vmatrix} 2 & 4 & -3 \\ -1 & 1 & 0 \\ 0 & 1 & -3 \end{vmatrix} = 2(-3) - 4(3) - 3(-1) = -6 - 12 + 3 = -15$$

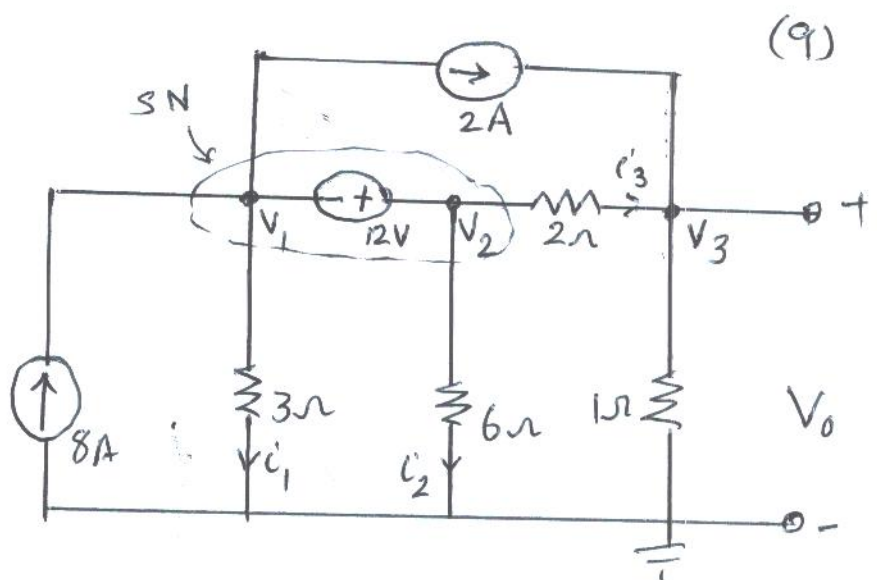
$$V_3 = \left(\frac{1}{-15} \right) \begin{vmatrix} 2 & 4 & 36 \\ -1 & 1 & 12 \\ 0 & 1 & -4 \end{vmatrix} = \frac{1}{-15} \{ 2(12) - 4(12) + 36(-1) \}$$



Problem (1)

Determine V_1, V_2


[Ans: $V_1 = -0.2V$
 $V_2 = (14/5)V$]

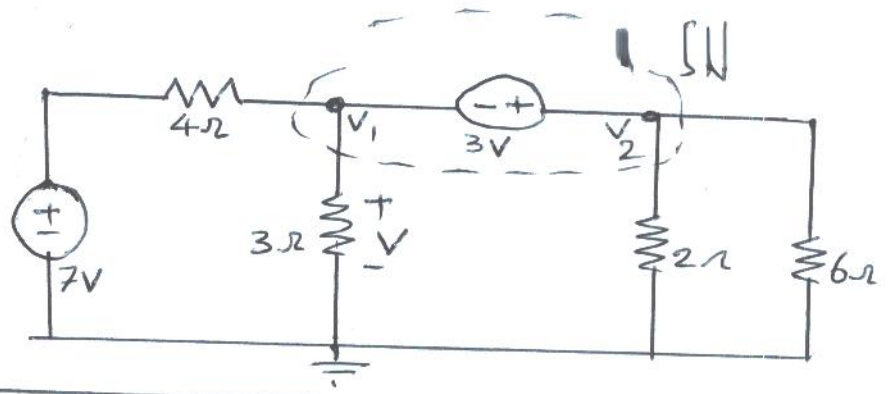

Problem (2)

Determine V_1, V_2


[Ans: $V_1 = 18V$
 $V_2 = 26V$]

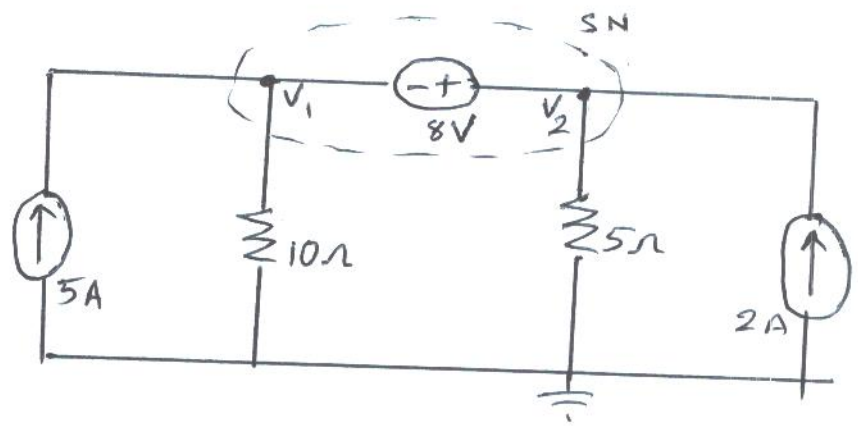

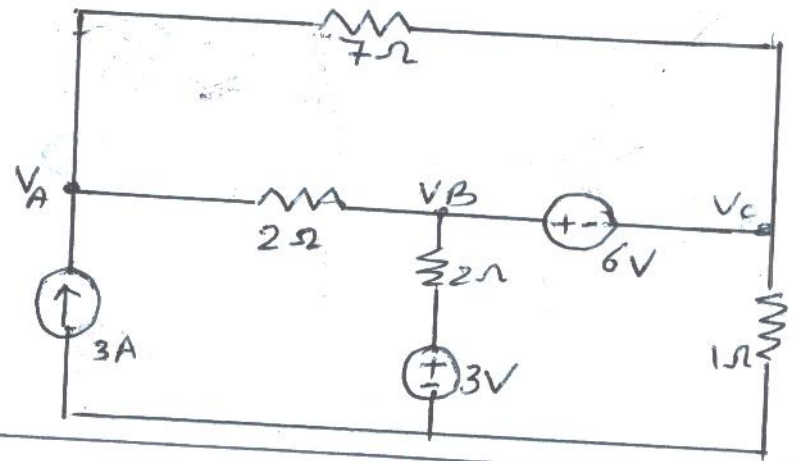Problem (3)

Find V_A, V_B and V_C

Ans [$V_A = 0.33V$
 $V_B = 7V$
 $V_C = 1V$]



Problem (4)

Ans [$V_1 = -7.333V$
 $V_2 = -5.333V$]

