

$$R = \frac{1}{\omega c} \rightarrow R = 20K\Omega,$$


$$5 = \frac{R_f}{R_1} \text{ let } R_f = 20K\Omega \rightarrow R_1 = 4K\Omega$$

Q5/: Design electronic circuit to solve the following Differential equation

$$\frac{d^2y}{dt^2} + 4\frac{dy}{dx} + 5y = 2\sin\omega t \text{ where } y(0) = 1\text{ volt and } \frac{dy}{dx}(0) = 0.5\text{ volt}$$

مبدأ الحل: أخلي المعادلة بدلاله اعلى مشتقه
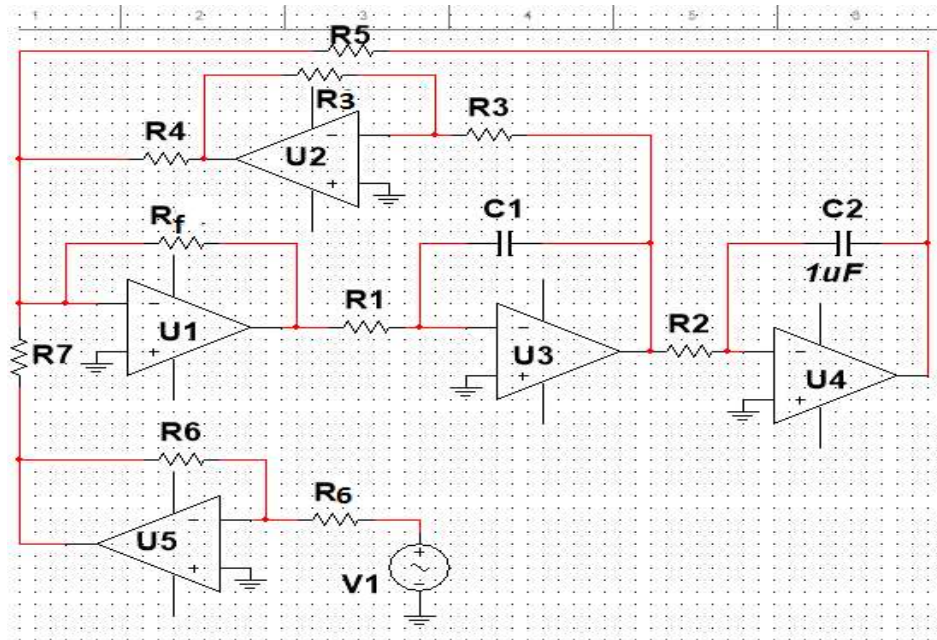
$$\frac{d^2y}{dt^2} = -4\frac{dy}{dx} - 5y + 2\sin\omega t$$



$$\frac{1}{R_1 C_1} = 1 \rightarrow \text{let } C_1 = 10\mu F \rightarrow R_1 = 100K\Omega$$


$$\frac{1}{R_2 C_2} = 1 \rightarrow \text{let } C_2 = 10\mu F \rightarrow R_2 = 100K\Omega$$

Let $R_3 = 100K\Omega$, Let $R_6 = 100K\Omega$

$$\frac{R_f}{R_4} = 4 \rightarrow \text{let } R_5 = 20K\Omega$$

$$\frac{R_f}{R_7} = 2 \rightarrow \text{let } R_7 = 50K\Omega$$

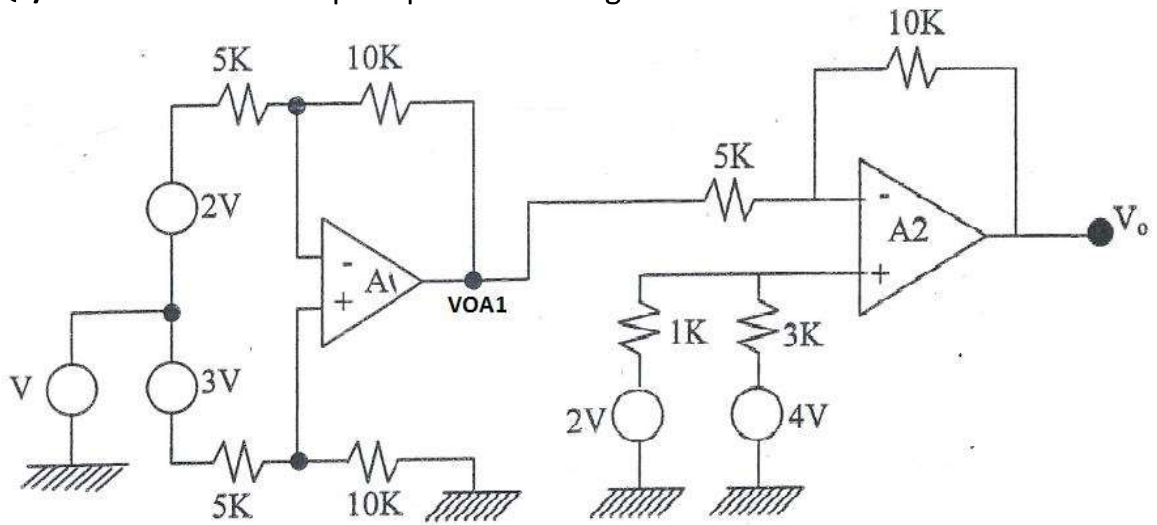Q6/: Find V_o from the op-amp showed in figure bellow



1- Differential op-amp


$$v_o = (v_2 - v_1) \times \frac{R_f}{R_1} \rightarrow = (3 - 2) \times \frac{10}{5} = 2 \text{ volt}$$

$$v_2 = \left(2 \times \frac{3}{4} + 4 \times \frac{1}{4} \right) = \frac{5}{2} \text{ volt} \quad (\text{super position})$$

2- Subtractor

$$v_o = \left(1 + \frac{R_f}{R_1} \right) v_2 - \frac{R_f}{R_1} v_1 \rightarrow = \left(1 + \frac{10}{5} \right) v_2 - \frac{10}{5} \times 2 = 3.5 \text{ volt}$$

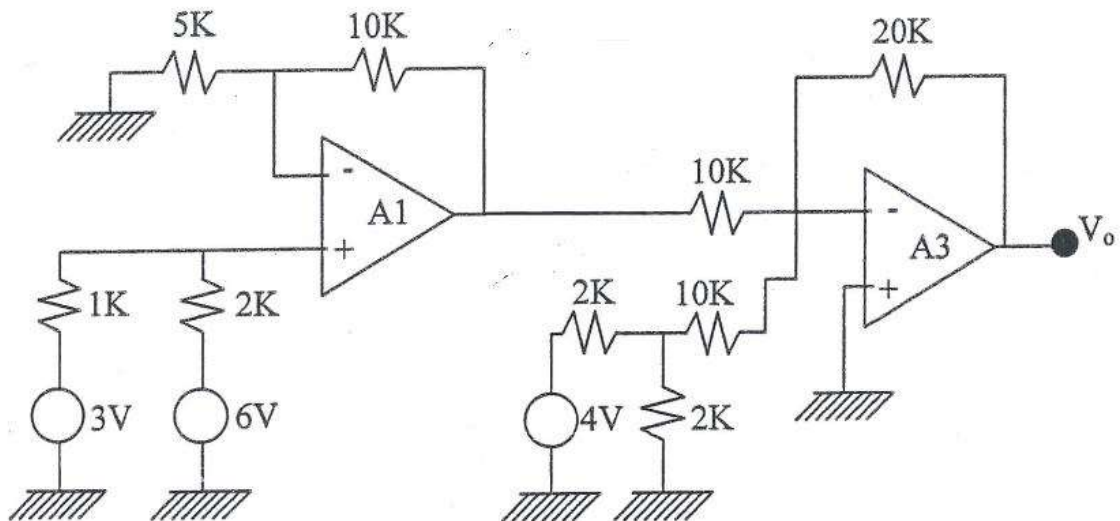Q6/: Find V_o from the op-amp showed in figure bellow



1- Adder


$$v_{oA1} = \frac{RA \times VB + RB \times VA}{RA + RB} \left(1 + \frac{Rf}{R1}\right) \rightarrow = \frac{3 \times 2 + 6 \times 1}{1 + 2} \left(1 + \frac{10}{5}\right) = 12 \text{ volt}$$

$$v_2 = \left(4 \times \frac{2}{4}\right) = 2 \text{ volt} \quad (\text{voltage divider})$$

2- Summing

$$v_o = -\left(\frac{Rf}{R1} v_1 + \frac{Rf}{R2} v_2\right) \rightarrow = -\left(\frac{20}{10} \times 12 + \frac{20}{10} \times 2\right) = -28 \text{ volt}$$

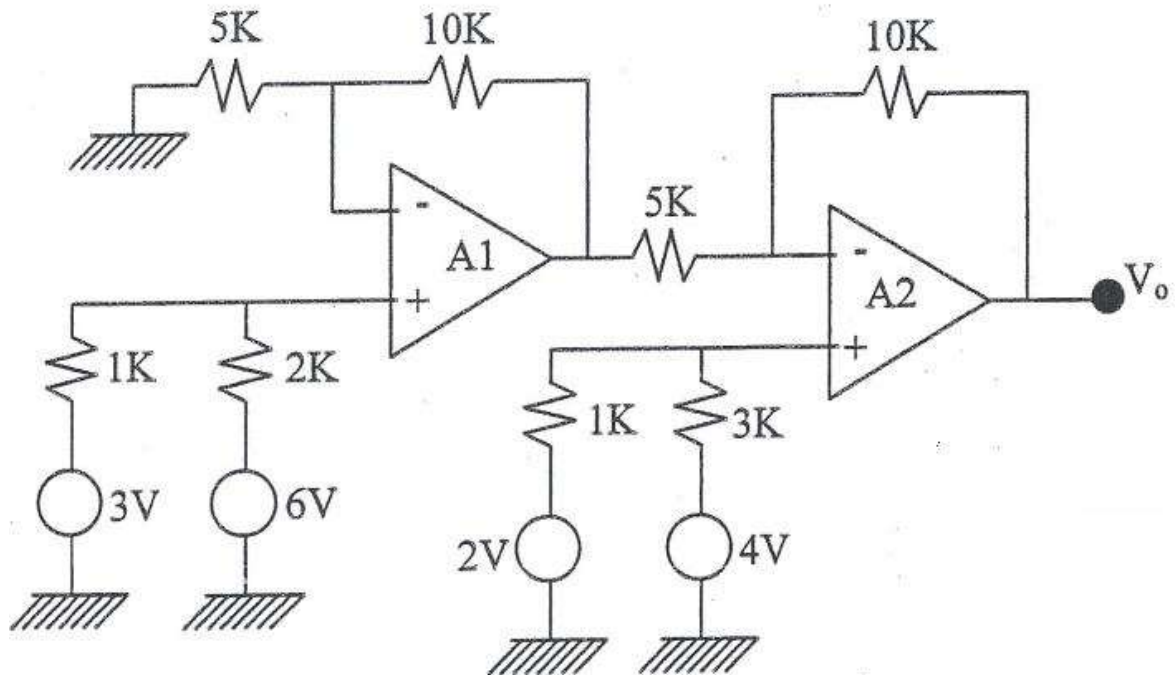Q7/: Find V_o from the op-amp showed in figure bellow



1- Adder


$$v_{oA1} = \frac{RA \times VB + RB \times VA}{RA + RB} \left(1 + \frac{Rf}{R1}\right) \rightarrow = \frac{3 \times 2 + 6 \times 1}{1 + 2} \left(1 + \frac{10}{5}\right) = 12 \text{ volt}$$

$$v_2 = \left(2 \times \frac{3}{4} + 4 \times \frac{1}{4}\right) = \frac{5}{2} \text{ volt} \quad (\text{super position})$$

2- Subtractor

$$v_o = \left(1 + \frac{Rf}{R1}\right) v_2 - \frac{Rf}{R1} v_1 \rightarrow = \left(1 + \frac{10}{5}\right) 2.5 - \frac{10}{5} \times 12 = -16.5 \text{ volt}$$

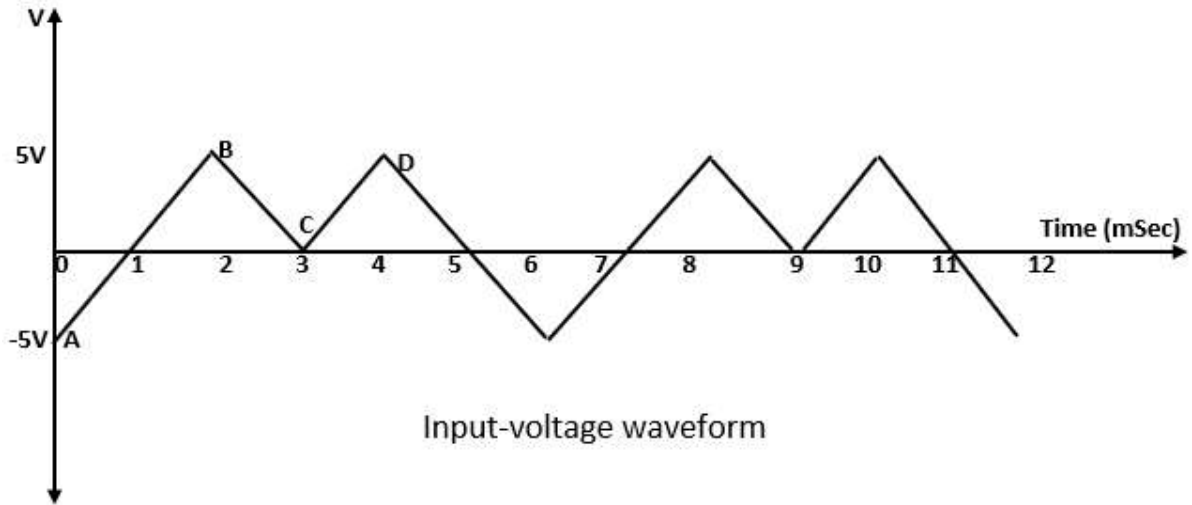Q8/: For the differentiator; if $R_f = 10K\Omega$ and the value of the capacitor is $0.001\mu F$, the input signal is given bellow. Find the output voltage waveform



$$(A) \quad \frac{dv_1}{dt} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{5 - (-5)}{2 \times 10^{-3} - 0} = 5 \times 10^3 \text{ v se}$$

c

