

# Chapter Eight

## AC TO AC Converters

## 8.1: Introduction: -

Ac-ac converters broadly define a set of power electronic topologies that are employed to obtain ac output of variable amplitude and frequency from fixed ac input without employment of bulky reactive components. A converter that gives variable amplitude ac is known as AC regulator or AC controllers and that employed for variable-frequency ac is known as cyclo-converter. Depending on the operation of thyristors, cyclo-converters can be naturally commutated (NCC) or forcefully commutated (FCC). Variation of the frequency in the NCC is restricted to only half of the supply frequency.

## 8.2 AC regulator or AC controllers

### 8.2.1: Single phase SCR full-wave AC-regulator

The current of SCR flow in only one direction, therefore two SCRs are connected in an inverse parallel configuration to control AC current.

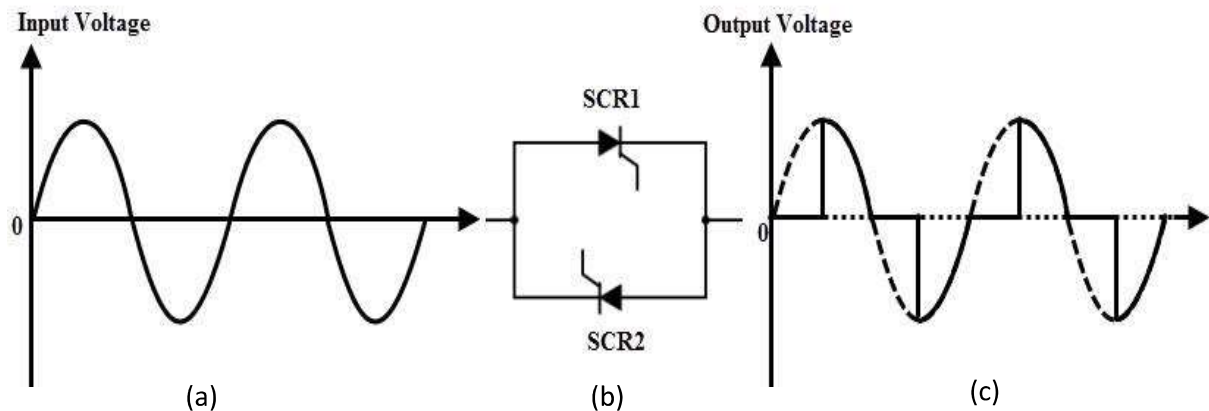



Fig. (8-1) AC back to back switch (a) input wave (b) power circuit (c) output wave

### Advantage of Back to back switch

- 1- Reliability
- 2- Low losses
- 3- Speedy turn-on and turn off

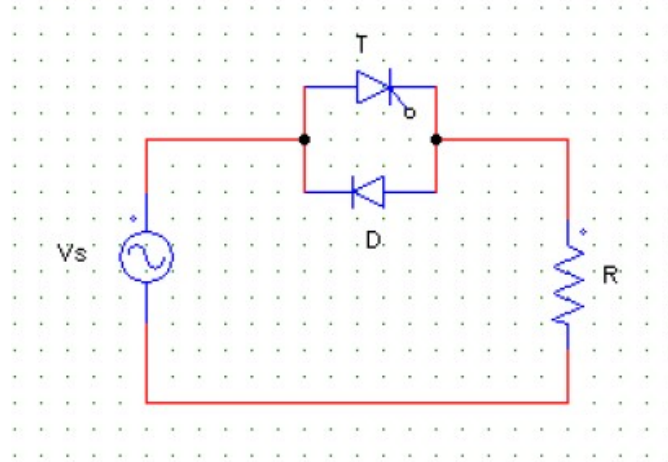
### 8.2.2: Single phase half-wave Ac-controller

This converter consists of an inverse parallel pair (SCR and Diode) as shown in figure bellow, also called THYRODE.



Working:

- In positive half cycle of AC supply SCR S is turn ON at  $\omega t = \alpha$ . during this load voltage is positive now SCR will be turn OFF due to natural commutation at  $\omega t = \pi$ . load current and source current are positive.
- In negative half cycle of AC supply Diode D1 will turn ON at  $\omega t = \pi$ . During these cycle load voltage is negative. and load current and source current are negative.
- By controlling the firing angle  $\alpha$  of the SCR we can control AC load voltage.

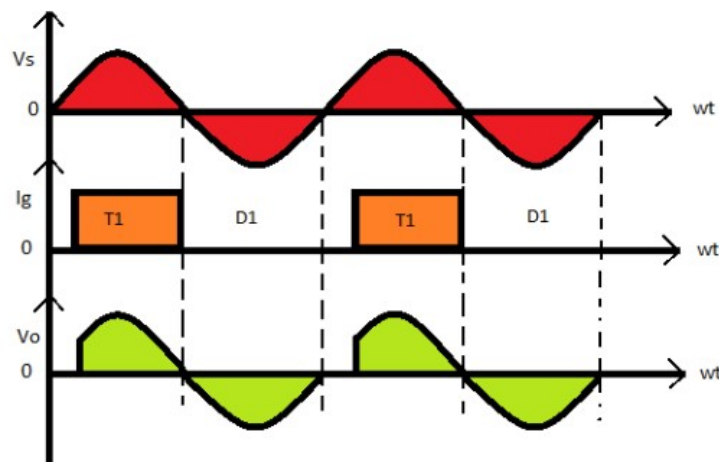

The conduction time is controlled by raring  $\alpha$

$$v_{o\ rms} = \frac{v_m}{\sqrt{2}} \left[ \frac{(\pi - \alpha) + 0.5 \sin(2\alpha)}{\pi} \right]^{0.5}$$

Power factor P.F =  $\frac{P_{o\ rms}}{V.A}$  where, A= the rms value of load current,

$$V = \frac{v_m}{\sqrt{2}}$$

$$p_{o\ rms} = \left[ \frac{(\pi - \alpha) + 0.5 \sin(2\alpha)}{\pi} \right]^{0.5}$$

The average value of SCR current

$$I_{scr} = \frac{I_m}{2\pi} [1 + \cos \alpha]$$

$$I_m = \frac{v_m}{R}$$

$$I_{scr} = \frac{V_m}{2\pi R} [1 + \cos \alpha]$$

EX.8-1] Thyristor AC Controllers with  $7\Omega$  resistive load is connected to ac voltage source  $v_{in} = 350 \sin 315t$ , if the conduction time of each thyristor is (2.5msec), calculate the load power.

**Ans.**

$$\phi_c = \omega \times t_c = 315 \times 2.5 \times 10^{-3} = 0.7875 \text{ rad} = 45^\circ$$

$$\alpha = 180 - \phi_c = 180 - 45 = 135^\circ = 2.354 \text{ rad}$$

$$v_{o\ rms} = \frac{v_m}{\sqrt{2}} \left[ \frac{(\pi - \alpha) + 0.5 \sin(2\alpha)}{\pi} \right]^{0.5}$$

$$v_{o\ rms} = \frac{350}{1.414} \left[ \frac{(3.15 - 2.354) + 0.5 \sin(2 \times 135)}{3.14} \right]^{0.5} = 75.3 \text{ v}$$

$$\text{The load power } p_L = \frac{V_{o\ rms}^2}{R} = \frac{75.3^2}{7} = 810 \text{ watts}$$