

Q3]3-Phase half -wave rectifier with delta-star transformer is connected to 10 Ω resistive load. For 220 V secondary line to line voltage and 50 Hz. Calculate

- 1- The dc load power 2- the conduction time of each diode.

Ans.

$$1) \quad P = \frac{V_{dc}^2}{R} \quad (1)$$

$$V_{dc} = \frac{3\sqrt{3}V_m}{2\pi} \quad (2)$$

$$V_m = \frac{\sqrt{2}}{\sqrt{3}} \times 220 \quad (3)$$

Sub. eq (3) in eq(2)

$$V_{dc} = \frac{3\sqrt{3} \times \frac{\sqrt{2}}{\sqrt{3}} \times 220}{2\pi} = 149 \text{ volt}$$

$$P = \frac{V_{dc}^2}{R} = \frac{149^2}{100} = 222 \text{ watts}$$

$$2) \quad T_c = \phi_c / \omega$$

$$T_c = \frac{2\pi}{3} / 2\pi 50 = 6.67 \text{ msec}$$

Q4]3-Phase half-wave rectifier with delta-star transformer and (250w,5A) resistive load. Find the value of the secondary line voltage.

Ans.

$$P_{dc} = V_{dc} \times I_{dc}$$

$$V_{dc} = \frac{250}{5} = 50 \text{ v}$$

$$V_{dc} = \frac{3\sqrt{3}V_m}{2\pi}$$

$$50 = \frac{3\sqrt{3} \times V_m}{2\pi} \rightarrow V_m = 60.5 \text{ v}$$

$$V_{rms,Line} = V_{max,phase} \times \frac{\sqrt{3}}{\sqrt{2}}$$

$$V_{rms,Line} = 60 \times \frac{\sqrt{3}}{\sqrt{2}} = 74 \text{ volt}$$

Q5]3-Phase bridge rectifier with delta-star transformer is connected to 10 Ω resistive load. For 220 V secondary line to line voltage and 50 Hz. Calculate

- 1- The dc load power 2- the conduction time of each diode.

Ans.

$$1) \quad P = \frac{V_{dc}^2}{R} \quad (1)$$

$$V_{dc} = \frac{3V_m}{\pi} \quad (2)$$

$$V_m = \sqrt{2} \times 220 \quad (3)$$

Sub. eq(3) in eq(2)

$$V_{dc} = \frac{3 \times \sqrt{2} \times 220}{\pi} = 297 \text{ volt}$$

$$P = \frac{V_{dc}^2}{R} = \frac{297^2}{100} = 883 \text{ watts}$$

$$2) \quad T_c = \phi_c / \omega$$

$$T_c = \frac{\pi}{3} / 2\pi 50 = 3.33 \text{ msec}$$

Q6]3-Phase bridge rectifier with delta-star transformer and (250w,5A) resistive load. Find the value of the secondary line voltage.

Ans.

$$P_{dc} = V_{dc} \times I_{dc}$$

$$V_{dc} = \frac{250}{5} = 50 \text{ v}$$

$$V_{dc} = \frac{3V_m}{\pi}$$

$$50 = \frac{3 \times V_m}{\pi} \rightarrow V_m = 52.33 \text{ v}$$

$$V_{rms,Line} = V_{max,phase} \times \frac{1}{\sqrt{2}}$$

$$V_{rms,Line} = 52.33 \times \frac{1}{\sqrt{2}} = 37 \text{ volt}$$

Q7]3-Phase Bridge rectifier with delta-star transformer and (2500w,25ohm) resistive load. Find the value of the secondary line voltage.

$$P = \frac{V_{dc}^2}{R}, V_{dc}^2 = P \times R,$$

$$V_{dc}^2 = 2500 \times 25$$

$$V_{dc}^2 = 625000, V_{dc} = 250\text{v}$$

$$V_{dc} = \frac{3V_m}{\pi}, 250 = \frac{3V_m}{\pi}, V_m = 261.67$$

$$V_{line} = \frac{V_m}{\sqrt{2}}, V_{line} = \frac{261.67}{\sqrt{2}} = 185\text{v}$$

Q8]3-Phase Bridge rectifier with $\Delta - Y$ transformer have DC Power of 500W and 5 Ω resistive load. Plot circuit diagram, then Find the value of the secondary line voltage.

$$P = \frac{V_{dc}^2}{R}, V_{dc}^2 = P \times R,$$

$$V_{dc}^2 = 500 \times 5$$

$$V_{dc}^2 = 2500, V_{dc} = 50 \text{ volt}$$

$$V_{dc} = \frac{3V_m}{\pi}, 50 = \frac{3V_m}{\pi}, V_m = 52.33$$

$$V_{line} = \frac{V_m}{\sqrt{2}}, V_{line} = \frac{52.33}{\sqrt{2}} = 37\text{v}$$

Q9]3-Phase half wave rectifier with $\Delta - Y$ transformer and (250w,10 Ω) resistive load. Plot circuit diagram, then Find the value of the secondary line voltage.

$$P = \frac{V_{dc}^2}{R}, V_{dc}^2 = P \times R,$$

$$V_{dc}^2 = 250 \times 10$$

$$V_{dc}^2 = 2500, V_{dc} = 50 \text{ volt}$$

$$V_{dc} = \frac{3\sqrt{3}V_m}{2\pi}, 50 = \frac{3\sqrt{3}V_m}{2\pi}, V_m = 60.5 \text{ volt}$$

$$V_{phase} = \frac{V_m}{\sqrt{2}}, V_{phase} = \frac{60.5}{\sqrt{2}} = 42.79 \text{ volt}$$

$$V_{line} = \sqrt{3} \times V_{phase} = 1.73 \times 42.79 = 74 \text{ volt}$$