


8.2.3 Single phase TRIAC AC Regulator

A triac is a bidirectional, three terminals dual, direction by applying a small current of either polarity between the gate and one of the two main terminals.

Triac is fabricated by integrating two thyristors in an inverse parallel connection

Use of triac

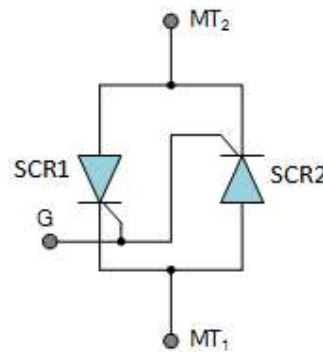- 1- Light dimming
- 2- Motor-speed control
- 3- Microcontroller power control



Advantage of using Triac

- 1- Triac are triggered by positive or negative polarity voltage applied at the gate terminal
- 2- A triac need a single heat sink of slightly large size, whereas anti-parallel thyristor pair need wo heat sinks of slightly smaller size

Disadvantage of using Triac

- 1- Triacs have low $\frac{dv}{dt}$ rating compare to the thyristor
- 2- Triacs are available in lower rating as compared to thyristor
- 3- Since a Triac can be triggered in either direction, a trigger circuit for triac careful consideration
- 4- The reliability of Triacs is lower than that of thyristor.

$$V_{o\ rms} = \sqrt{\frac{n}{K}} \times V_{rms}$$

$$P.F = \sqrt{\frac{n}{K}} \quad \text{Where, } \frac{n}{K} = \text{duty cycle}$$

EX.8-2] Triac AC controller supplies electrical furnace of 8Ω heating element, for 240 v, 50Hz voltage supply, the control circuit is an integral cycle control circuit that allows the current to flow for 2 cycles on and be off 1 cycle.

Calculate: - 1- The load power 2- The supply power factor

Ans.

$N=2$ and $M=1$

$K = 2+1 =3$

$$p_L = \frac{V_{(orms)}^2}{R} = \frac{(\sqrt{\frac{n}{K}} \times V_{rms})^2}{8}$$

$$= \frac{(\sqrt{\frac{2}{3}} \times 240)^2}{8} = 4800 \text{watts}$$

$$P.F = \frac{P_L}{P_{in}} = \frac{V_{orms}}{v_{rms}} = \sqrt{\frac{n}{K}} = \sqrt{\frac{2}{3}} = 0.816$$