

2.3 BJT Switching Times

Consider the BJT Switching circuit shown in Fig.(2.5), the BJT is at the cutoff region when the input signal at level V_{BB} and at the saturation region at level $-V_{BB}$. when the switch is transformed from level V_{BB} to level $-V_{BB}$ the response of the circuit will be as shown in fig.(2.6).

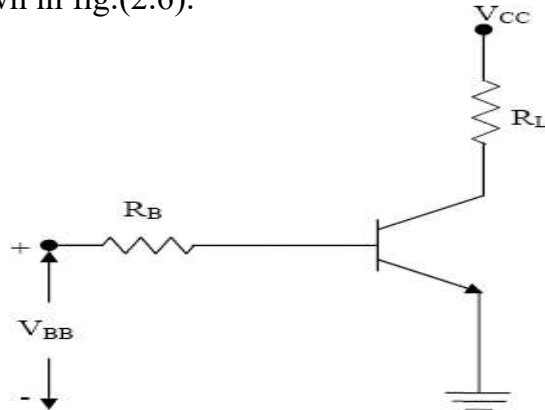


Fig. (2-5) Common emitter BJT switch

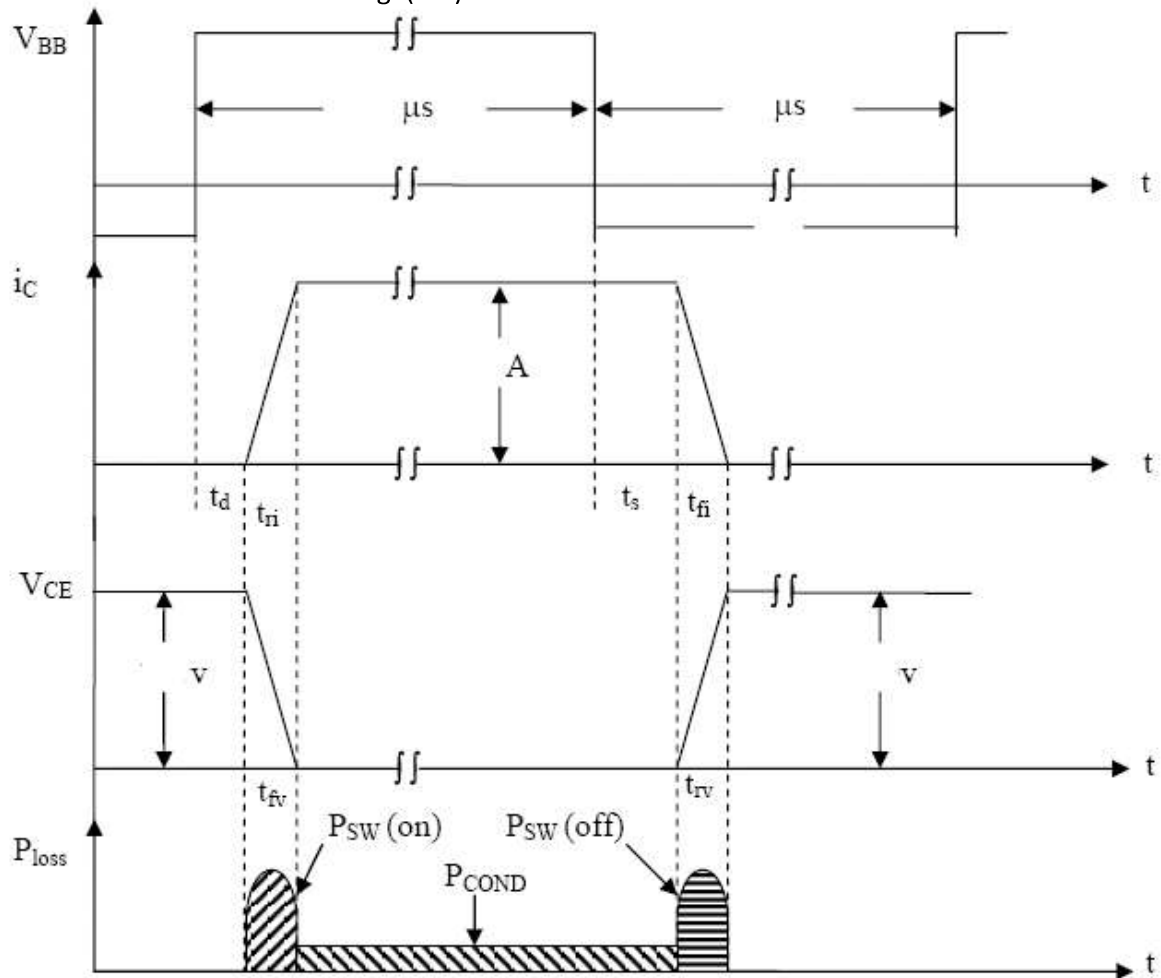


Fig. (2-6) Switching time specifications of common emitter BJT switch

The Switching Times of BJT are: -

1- Delay time

= t_d is the time period required for I_C to become 10% of $I_{C(sat)}$ when the input pulse is applied

2- Rise time

= t_r is the time period required for I_C to rise from 10% of $I_{C(sat)}$ to 90% of $I_{C(sat)}$

3- Turn-on time $t_{on} = t_d + t_r$

4- Storage time

= t_s is the time period required for I_C to fall to 90% of $I_{C(sat)}$ when the input pulse falls from V_{BB} to $-V_{BB}$

5- Fall time

= t_f is the time period required for I_C to fall from 90% of $I_{C(sat)}$ to 10% of $I_{C(sat)}$

6- Turn-off time $t_{off} = t_s + t_f$

The switching times can be improved by shunting the base resistance R_B with capacitor C_{su} called speed up capacitor

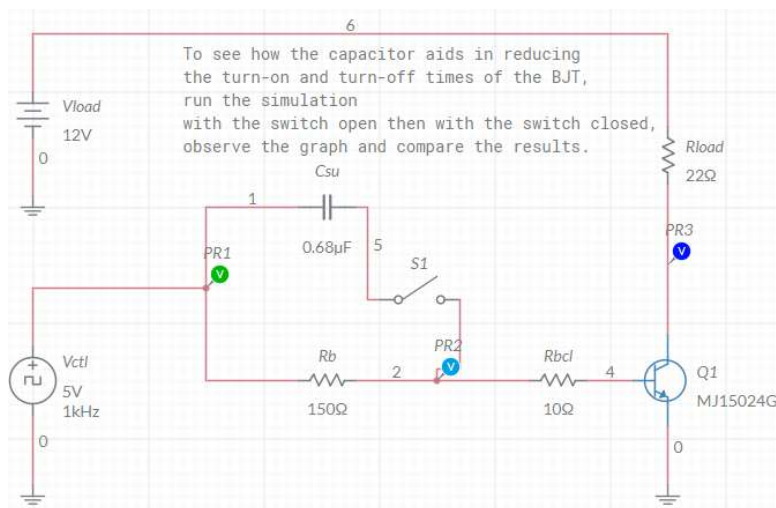


Fig. (2-7) Common emitter BJT switch with speed up capacitor

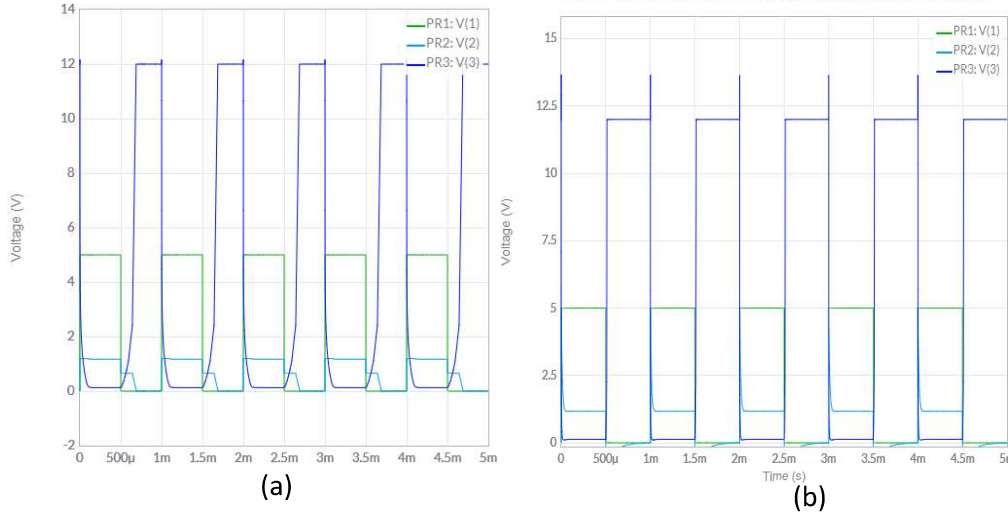


Fig. (2-8) output of Common emitter BJT switch (a) without speed up capacitor, (b) with speed up capacitor

2.4 BJT Switching Energy Losses

القدرة الكلية المفقودة = القدرة المفقودة بسبب الحرارة + القدرة المفقودة بالمفتاح

$P_{heat} = P_{Sat}$ القدرة المفقودة بسبب الحرارة = القدرة الخاصة بالتشبع

P_{MS} القدرة المفقودة بالمفتاح = تردد المفتاح \times طاقة المفتاح

Total power losses = Heat power losses + Switching power losses

$$P_{total} = P_{Sat} + P_{MS}$$

$$P_{heat} = P_{Sat} = V_{CE} \times I_C$$

$$P_{MS} = W_S \times f_C$$

P_{MH} القدرة المعالجة

$$P_{MH} = V_{CC} \times I_C$$


الطاقة المفقودة بالمفتاح = الطاقة المفقودة بالتشغيل + الطاقة المفقودة بالإطفاء

$$W_S = W_{on} \times W_{off}$$

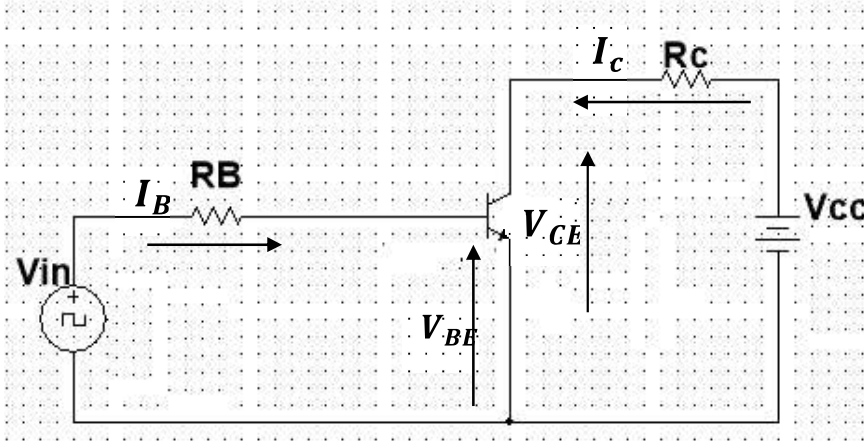2.5 Summary

* في هذا الفصل نوعين من الدوائر التي تستخدم الترانسيستور كمفتاح

اولا : دائرة المفتاح كامل التشغيل Fully driven BJT switching



تعتبر هذه الدائرة غير مثالية وذلك لوجود خسائر بشكل حرارة متمثلة بقيمة ال V_{CE} وعلية فأن القوانين المستخدمة للحل تكون

$$I_c = I_{sat} = \frac{V_{cc} - V_{ce}}{R_c}$$


$$I_{Bmin} = \frac{I_{c(sat)}}{B_{dc}}$$

Condition of operation

$$I_B = 3 \times I_{Bmin}$$

$$V_{in} = I_B R_B + V_{BE}$$

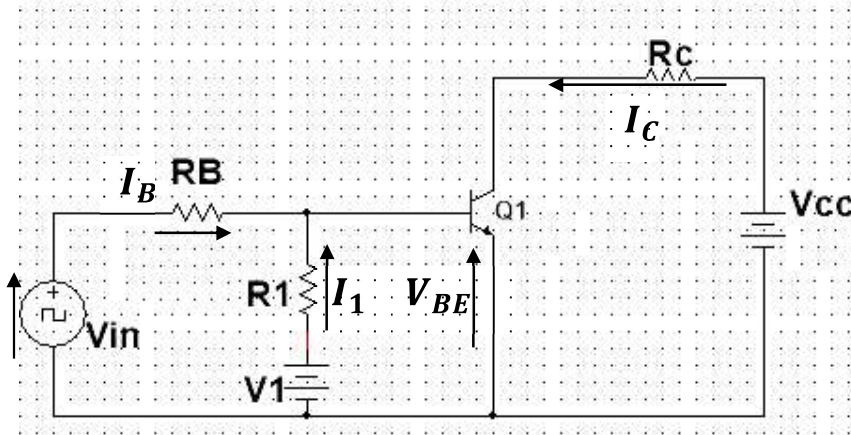ثانيا : دائرة المفتاح فوق التشغيل Over driven BJT switching



تعتبر هذه الدائرة مثالية وذلك لعدم وجود خسائر $V_{CE} = 0$ وعلية فإن القوانين المستخدمة للحل تكون

$$I_c = I_{max} = \frac{V_{cc}}{R_c}$$

$$I_{Bmin} = \frac{I_{max}}{B_{dc}},$$

Condition of operation

$$I_B = I_{Bmin}$$

$$I_1 = 2 \times I_B$$

$$V_{in} = I_B R_B + V_{BE}$$

$$V_1 = I_1 R_1 + V_{BE}$$

2.6 Exercises and Problems

Q1] An ideal common emitter NPN BJT switching circuit , for $V_{cc} = 25v$ and the control signal $I_B = 0.1 mA$, find the value of R_c if $B_{dc} = 50$.

Ans.

$$I_{Cmax} = I_c = B_{dc} \times I_B = 50 \times 0.1 = 5 mA$$

$$R_c = \frac{V_{cc}}{I_c} = \frac{25}{5 \times 10^{-3}}$$