

Q2] For the following circuit find the value of RB

Ans


$$V_{CE(sat)} = 150 \times 10^{-3} = 1.5 \text{ volt}$$

$$I_c = I_{sat} = \frac{V_{cc} - V_{CE}}{R_c}, I_c = \frac{30 - 0.15}{2 \times 10^3} = 14.9 \text{ mA}$$

$$I_{Bmin} = \frac{I_{c(sat)}}{B_{dc}}, I_c = \frac{14.9 \times 10^{-3}}{45} = 0.33 \text{ mA}$$

$$I_B = 3 \times I_{Bmin} = 3 \times 0.33 = 0.99 \text{ mA}$$
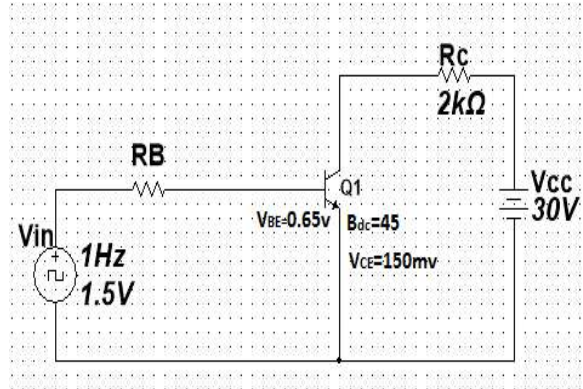
$$V_{in} = I_B R_B + V_{BE} = 0, R_B = \frac{V_{in} - V_{BE}}{I_B}, R_1 = \frac{1.5 - 0.65}{1 \times 10^{-3}} = 850 \Omega$$



Q3] For the following circuit Find

- 1- The value of R1
- 2- The value of Vin

Ans

$$I_c = \frac{V_{cc} - V_{CE}}{R_c}, I_c = \frac{20 - 0}{2 \times 10^3} = 10 \text{ mA}$$

$$I_c = \frac{I_c}{B_{dc}}, I_c = \frac{10 \times 10^{-3}}{100} = 100 \times 10^{-6}$$

$$I_1 = 2 \times I_{Bmin} = 2 \times 100 \times 10^{-6} = 200 \times 10^{-6}$$


$$V_1 - R_1 I_1 - 0.7 = 0, R_1 = \frac{V_1 - 0.7}{I_1}, R_1 = \frac{5 - 0.7}{200 \times 10^{-6}} = 21.5 \text{ K}\Omega$$

$$V_{in} - R_B I_B - 0.7 = 0,$$

$$V_{in} = R_B I_B + 0.7,$$

$$V_{in} = 10 \times 10^3 \times 100 \times 10^{-6} - 0.7$$

$$V_{in} = 1.7 \text{ V}$$

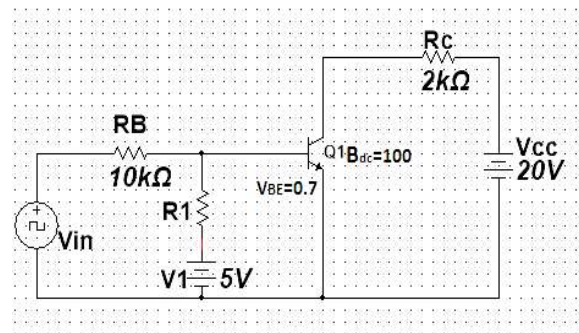

Q4] A common emitter NPN BJT switching circuit has the following data : $V_{CC}= 100V$, $V_{CE}= 200mV$, Maximum power handling of 1KVA, Maximum switching energy 5Mj, and total power dissipation = 52w. Find the value of switching frequency.

Ans

$$P_{ms} = w_s \times f_s$$

$$P_{total} = P_{heat} + P_{ms}$$

$$P_{ms} = P_{total} - P_{heat}$$

$$P_{heat} = V_{CE} \times I_C$$

$$P_{MS} = V_{CC} \times I_C \rightarrow I_C = \frac{P_{MS}}{V_{CC}} = \frac{1000}{100} = 10A$$

$$P_{heat} = V_{CE} \times I_C = 200 \times 10^{-3} \times 10 = 2 \text{ watt}$$

$$P_{ms} = 52 - 2 = 50 \text{ watt}$$

$$50 = 5 \times 10^{-3} \times f_s$$

$$f_s = \frac{50}{5 \times 10^{-3}} = 10000 \text{ Hz}$$

Q5] A common emitter NPN BJT switching circuit has the following data : $V_{CC}= 100V$, $V_{CE}= 200mV$, Maximum power handling of 1KVA. (1) Find the value of R_C (2) calculate the maximum power dissipated as a heat.

Ans

$$P_{MS} = V_{CC} \times I_C = 1 \times 10^3 = 1000VA$$

$$I_C = \frac{P_{MS}}{V_{CC}} = \frac{1000}{100} = 10A$$

$$R_C = \frac{V_{CC} - V_{CE(sat)}}{I_C} = \frac{100 - 200 \times 10^{-3}}{10} = 9.9\Omega$$

$$P_{heat} = P_{sat} = V_{CE} \times I_C = 200 \times 10^{-3} \times 10 = 2 \text{ watts}$$