

$$V_C = V_E = V_P = V_D + \eta V_{BB} \quad (4)$$

For ideal diode $V_D = 0$

$$V_P = \eta V_{BB} \quad (5)$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}} \quad (6)$$

- اذا طلب بالسؤال اقصى تردد maximum frequency يعني يجب استخراج اقل زمن minimum time واقل مقاومة R_{min} وتكون القوانين كالآتي

$$F_{max} = \frac{1}{T_{min}} \quad (1)$$

$$T_{min} = R_{min} C_1 L n \frac{1}{1 - \eta} \quad (2)$$

$$R_{min} = \frac{V_{BB} - V_V}{I_V} \quad (3)$$

- اذا طلب بالسؤال اقل تردد minimum frequency يعني يجب استخراج اقل زمن maximum time واقل مقاومة R_{man} وتكون القوانين كالآتي

$$F_{min} = \frac{1}{T_{max}} \quad (1)$$

$$T_{max} = R_{max} C_1 L n \frac{1}{1 - \eta} \quad (2)$$

$$R_{max} = \frac{V_{BB} - V_p}{I_p}$$

- اذا لم يعط قيمة V_p نستخرجها من العلاقة التالية

$$V_P = V_D + \eta V_{BB}$$

3.6 Exercises and Problems

Q1] A UJT (UNJUNCTIONAL TRANSISTOR) is used as a relaxation oscillator where $V_{BB}=20v$, $I_V= 10mA$, $V_V= 0.6v$, $I_p=40\mu F$, $C_1=1\mu F$, and $\eta = 0.65$. Find the value of maximum and minimum frequency.

Ans

$$R_{1min} = \frac{V_{BB} - v_V}{I_V} = \frac{20 - 0.6}{10 \times 10^{-3}} = 19.4 \times 10^2$$

$$T_{min} = R_{1min} C_1 \ln\left(\frac{1}{1-\eta}\right)$$

$$= 19.4 \times 10^2 \times 1 \times 10^{-6} \ln\left(\frac{1}{1-0.65}\right) = 2.035 \times 10^{-3}$$

$$F_{max} = \frac{1}{T_{min}}, F_{max} = \frac{1}{2.035 \times 10^{-3}}, F_{max} = 492.6Hz$$

$$v_p = \eta V_{BB} = 0.65 \times 20 = 13volt$$

$$R_{1max} = \frac{V_{BB}-v_p}{I_p} = R_{1min} = \frac{20-13}{40 \times 10^{-6}} = 1.7 \times 10^5 \Omega$$

$$T_{max} = R_{1max} C_1 \ln\left(\frac{1}{1-\eta}\right)$$

$$= 1.75 \times 10^5 \times 1 \times 10^{-6} \ln\left(\frac{1}{1-0.65}\right) = 1.83575sec$$

Q2] A UJT (UNJUNCTIONAL TRANSISTOR) has the following data: $V_{BB}=30v$, $R_1=100K\Omega$, $V_D=0.6v$, $\eta = 0.65$.

- 1- What is the value of C_1 that gives 1KHz output frequency?
- 2- Calculate the maximum value of the capacitor voltage.

Ans

$$F_{max} = \frac{1}{T_{min}} = \frac{1}{1 \times 10^{-3}} = 1 \times 10^3$$

$$T_{min} = R_{1min} C_1 \ln\left(\frac{1}{1-\eta}\right)$$

$$1 \times 10^{-3} = 1 \times 10^3 \times C_1 \ln\left(\frac{1}{1-0.6}\right), C_1 = 0.01\mu F$$

$$V_c = V_p = V_D + \eta V_{BB} = 0.6 + (0.6 \times 30) = 18.6 volt$$

Q3] A UJT (UNJUNCTIONAL TRANSISTOR) is used as a relaxation oscillator where $V_{BB}=12\text{V}$, $I_V= 11.4\text{mA}$, $V_v= 0.6\text{V}$, $C_1=1\mu\text{F}$, and $\eta = 0.65$. Find the value of maximum frequency.

Ans

$$F_{max} = \frac{1}{T_{min}}$$

$$R_{1min} = \frac{V_{BB}-v_V}{I_V} = R_{1min} = \frac{12-0.6}{11.4 \times 10^{-3}} = 1K\Omega$$

$$T_{min} = R_{1min} C_1 \ln\left(\frac{1}{1-\eta}\right) = 1 \times 10^3 \times 1 \times 10^{-6} \ln\left(\frac{1}{1-0.65}\right), T_{min} = 1.049 \text{ msec}$$

$$F_{max} = \frac{1}{1.049 \times 10^{-3}}, F_{max} = 953.3 \text{ Hz}$$

Q4] A UJT (UNJUNCTIONAL TRANSISTOR) is used as a relaxation oscillator where $V_{BB}=30\text{V}$, $R_1=100K\Omega$, $C_1=10\mu\text{F}$, and $\eta = 0.6$. Find the value of frequency.

Ans

$$F = \frac{1}{T}$$

$$T = R_1 C_1 \ln\left(\frac{1}{1-\eta}\right) = 100 \times 10^3 \times 1 \times 10^{-6} \ln\left(\frac{1}{1-0.6}\right), T = 0.916 \text{ sec}$$

$$F = \frac{1}{0.916}, F = 1.09 \text{ Hz}$$

Q5] Sketch the input forward characteristic curve of UJT and point to the regions of operation.

Q6] Fill the following blanks with the suitable words:-

- 1- UJT is also called double ----- and -----
- 2- Intrinsic stand off ratio is the coefficient of UJT of typical value lies between -- ----- and -----.
- 3- UJT interbase resistance of N block of several thousand of ohms when positive voltage is applied to -----at -----=0.
- 4- Condition of operation of UJT is -----
- 5- The UJT has three operation regions, they are -----, -----and-----
- 6- The oscillation condition of UJT oscillator is -----.
- 7- The voltage on the charging capacitor may be expressed by -----.