



المادة: مبادئ الالكترونيك
الصف: الاول / صباحي
الزمن: ثلاثة ساعات
التاريخ: ١٢ / ١١ / ٢٠١٩

اسئلة الامتحان النهائي للعام الدراسي 2018/2019 الدور الثاني

ملاحظة: أجب عن اربعة اسئلة فقط

السؤال الأول:

- (أ) عدد تيار انحصار العكسى للبلورة مع الشرح
(ب) وضح مع الرسم عملية تعليم ذرات السليكون للحصول على شبه موصل موجب

(15) درجة

السؤال الثاني:

عرف ما ياتي

- (أ) ١- حزمة التكافوء ٢- تيار الثنائي الاعظم ٣- التوحيد ٤- ثانوي زينر ٥- الايون

(10) درجات

- (ب) وضح مبدأ عمل المقام المنحاز الموجب مع الرسم

السؤال الثالث:


- (أ) وضح مناطق عمل الترانزستور مع الرسم

(10) درجات


- (ب) وضح عمل موحد الموجة القطرى مع رسم الدائرة وإشارة الارجاع

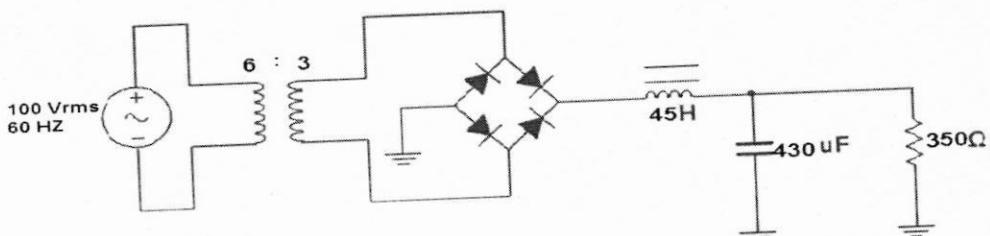
(15) درجة

- السؤال الرابع: في دائرة المرشح الموضحة أدناه، إذا كانت مقاومة الخانق المستمر $\Omega = 50$. احسب
ـ فولتية الإرجاع المستمرة ـ تموج الإرجاع ـ عامل التموج ـ المحاثة الحرجة Lcritical ـ ارسم اشاره تموج
الإرجاع.



 - السؤال الخامس: في دائرة انحصار الباعث ادناء. احسب IC و VCE وكذلك ارسم خط الحمل المستمر
وعين احداثيات نقطة العمل Q



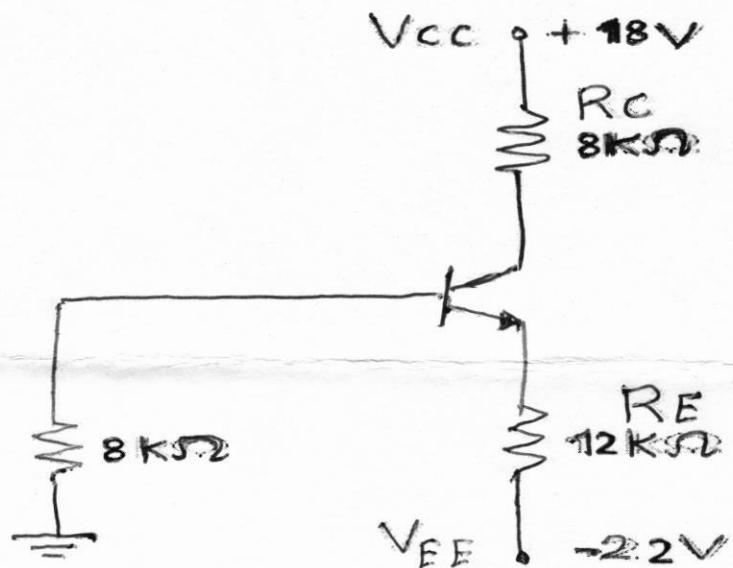

((تمنياتنا لطلبتنا الأعزاء بالتوفيق والنجاح))


رئيس القسم
م.م. كرار سالم عباس


مدرس المادة
م.م. احسان محسن عبيد

VANCOUVER

1950

1950

RE

1950

1950

RE

1950

وزارة التعليم العالي والبحث العلمي
جامعة التقنية الجنوبية
المعهد التقني / القرنة
قسم التقنيات الكهربائية



المادة: التأسيسات الكهربائية (2)
الصف: الثاني / صباحي
الزمن: ثلاثة ساعات
التاريخ: ١٢ / ١١ / ٢٠١٩

اسئلة الامتحان النهائي للعام الدراسي 2018/2017 نموذج رقم (2) الدور-الثالث

ملاحظة: أجب عن خمسة أسئلة فقط

(20) درجة

- أ- عرف ما يلي 1- المواد الموصلة 2- الشبكة الأرضية 3- الميكا 4- الصواعق 5- قاطع الدورة
ب-وضح كيف تكون الصواعق بالتفصيل مع الرسم؟

(20) درجة

السؤال الثاني:

- أ- حول كل مما يأتي 1- (412 °C) الى فهرنهايتية 2- (14 °C) الى فهرنهايتية 3- (200F°) الى سيلزية

ب- سخان 3 كيلو واط متصل بخزان معدني يحتوي على 113,65 لتر من الماء فإذا كانت درجة حرارة الماء الابتدائية 27°C فما هو الوقت الازم لكي تصل درجة الحرارة للماء 77°C أولاً بافتراض انه لا يوجد فقد بالحرارة، ثانياً بافتراض الكفاءة 80%, علماً ان الحرارة النوعية للماء هي 4190.

(20) درجة

السؤال الثالث:

- أ- حمل ثلاثي الاطوار متزن (300Kw) يتغذى من مصدر (415v) على معامل قدرة (0.78) متاخر من خلال قابلو نحاسي ثلاثي طوله (260m) ومساحة مقطع قلب كل قابلو (400mm²). احسب قيمة هبوط الجهد في القابلو، علماً ان مقاومة النحاس (0.017μΩ.m).

ب- عرف الارضي (التاريس)، وما هي مميزات الارضي الجيد ، وما هي شروط الحصول على الارضي الجيد؟

(20) درجة

السؤال الرابع:


- أ- لدينا ثلاثة احمال متوازية الحمل الاول (يمتلك قدرة 100 واط وعامل قدرة 0.92 متاخر) الحمل الثاني (يمتلك قدرة 250 واط وعامل قدرة 0.85 متاخر) الحمل الثالث (يمتلك قدرة 150 واط وعامل قدرة 1) احسب التيار الكلي للمصدر وعامل القدرة الكلي اذا كانت فولتية الخط 115 فولت.

ب- إذا كانت قائمة أجور الكهرباء لتجهيز معين هي كالتالي:

القراءة السابقة	القراءة اللاحقة	تاريخها	تاريخها	رقم الحساب
؟	/	47491	/	415
تاريخ الاصدار	المبلغ الحالي	الديون	المجموع المطلوب	10 دينار عراقي
/	؟	12000	19290	10 دينار عراقي

ب- جد القراءة السابقة علماً انه يتم حساب الفاتورة كالتالي

10 دينار عراقي	500-1
10 دينار عراقي	1000-501

 

السؤال الخامس:

- (10) درجة
(10) درجة

أ- عدد انواع قواطع الدورة من حيث جهد التشغيل
ب- ماذا نعني بفترة التأخير في مناولات الجهد

السؤال السادس:


أ- قضيب ارضي مدفن طوله 3متر وقطرة 50ملم، اجريت عليه فحوصات بواسطة جهاز وينر بأمرار تيار مقداره 5 امبير واستلام جهد 25 فولت، إذا كانت المسافة بين اقطاب الجهاز (A) تعطى بالعلاقة التالية $A = 2 \times B + 5$ وعمق مسامير الجهاز (B) هو 2 متر. احسب مقاومة القضيب.

ب- مصباح متوج يعطي اضاءة الى الاسفل على سطح منضدة، هذه الاضاءة عمودية على هذا السطح مقدارها (63.5 lux)، هذه الشاشة حركت افقيا بمقدار 1.3 متر على المنضدة ، فان الاضاءة أصبحت (38.8 lux) احسب قدرة المصباح بالشمعة (I) وكذلك المسافة العمودية من المصباح الى المنضدة.

رئيس القسم
كرار سالم عباس

((تمنياتنا لطلبتنا الأعزاء بالتوفيق والنجاح))

 مدرس المادة
عبد الغفور عبد الغفار عبد الحميد





Final Exam 2018/2019 - Model no. (3) – (٣) Attempt

Note: Answer Four Questions only

Q1/ Convert the following numbers

(25 Mark)

$$\begin{array}{lll} 1- (432.34)_8 = (...)_{10} & 2- (348.235)_{10} = (...)_8 & 3- (101001001)_2 = (...)_{16} \\ 4- (623.543)_8 = (...)_{16} & 5- (EF.3C)_{16} = (...)_8 \end{array}$$

Q2/A- subtract $(111)_2$ from $(1110)_2$ using the 2nd complement

(12 Mark)

B-Draw the logic circuit and write the truth table of Half Adder circuit

(13 Mark)

Q3/A-Draw the logic NAND gate and write the truth table and the wave forms **(10 Mark)**

B-For J-K Flip Flop, draw the logic circuit and write its truth table and draw the wave forms **(15 Mark)**

Q4/A-Write the Boolean expression and Draw the logic circuit for the Following table

(10 Mark)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

B-Convert the standard SOP to POS and draw the logic circuit of POS

(15 Mark)

$$Y = (ABC) + (\overline{A} B \overline{C}) + (A \overline{B} \overline{C}) + (\overline{A} \overline{B} C) + (\overline{A} \overline{B} \overline{C})$$

TURN THE PAGE

ball, a red one

Ministry of Higher Education &
Scientific Research
Southern Technical University
Technical Institute / Qurna
Dept. of Electrical Techniques



Subject: Digital Electronics
Class: First – Morning
Time: Three Hours
Date: / / 2019

Q5/A- Simplify the following expression using the Boolean rules (10Marks)

$$Y = AB + A(B+C) + B(B+C)$$

B- Use karnough map to simplify the Boolean expression and draw the logic circuit for the truth table below (15 Mark)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

Examine

Assist. Lect. Ehsan Mohsin

BEST OF LUCK


Head of department

Karar S. Abbas





اسئلة الامتحان النهائي للعام الدراسي 2018/2019 الدور الثالث

ملاحظة: اجب عن جميع الاسئلة (كل سؤال 20 درجة/كل فرع 10 درجات)

١) اجب عن فرعين فقط:

- (أ) عدد بالتفصيل أنواع محطات توليد الطاقة الكهربائية (وضح بالرسم اثنين منها فقط).
 (ب) ما هي محسن وعيوب الطاقة الشمسية.
 (ج) ما هي أنواع شبكة توزيع القدرة الكهربائية؟ صنفها اعتماداً على مقدار فولتية التوزيع.

س²

- أ) كيف تؤثر العوامل التالية على خطوط النقل:
 ١- الموصلية ٢- المثانة الميكانيكية ٣- معامل المرونة ٤- الكلفة؟

(ب) ما هي محسن ومساوٍ نقل القدرة الكهربائية بفولتيات مستمرة؟

س³

- أ) ما هي أنواع الموصلات المستخدمة في خطوط النقل الكهربائية؟ عددها واشرح اثنين منها.

(ب) خط نقل كهربائي هوائي ثلاثي الاطوار طوله (50km) يجهز حمل بقدرة (5MW) عند جهد (22kV) وعامل قدرة (0.8Lag) متأخر. مقاومة الخط (Ω) ٤ والممانعة الحثية للخط (Ω) ٦. احسب تنظيم الفولتية وكفاءة النقل.


س⁴

- أ) خط نقل متوسط ممثل بطريقـة (T) ارسم الدائرة المكافـفة والمخطط الطوري له وكيف يمكن حساب فولـtieـة الارسـال .(V_s)

(ب) ما هي العوامل التي تؤثر على تدلي الاسلاك في خطوط نقل الطاقة الكهربائية.

س⁵

 - أ) سلسلة عزل لخط نقل كهربائي هوائي مكونة من خمس وحدات عزل اشتق الفولتية على الوحدة الخامسة.




س⁵

ب) خط نقل كهربائي هوائي ثلاثي الاطوار طوله (110km) يجهز حمل بقدرة (50MW) عند جهد (110kV) وتردد (50Hz) وعامل قدرة (0.8Lag) متأخر. ويمثل التوايت التالية لكل طور: مقاومة الخط (15Ω) والممانعة الحثية للخط (6Ω) والمسايرة (المسامحة) السعوية للخط ($S^{5*} 45^\circ$). احسب فولتية الارسال وتيار الارسال على فرض ان الخط ممثلا بطريقه π .

((تمنياتنا لطلبتنا الأعزاء بالتوفيق والنجاح))

رئيس القسم
م.م. كرار سالم عباس

 مدرس المادة
م.م. زين الدين سعيد عبد الرحمن



وزارة التعليم العالي والبحث العلمي
جامعة التقنية الجنوبية
المعهد التقني / القرنة
قسم التقنيات الكهربائية



المادة: الرياضيات
الصف: الاول / صباحي
الزمن: ثلاثة ساعات
التاريخ: ٢٠١٩ / ١١ / ١٥

اسئلة الامتحان النهائي للعام الدراسي ٢٠١٩/٢٠١٨ نموذج رقم (١) الدور الثالث

ملاحظة: أجب عن جميع الأسئلة

(٢٠) درجة

$$(1) \quad y = \frac{3x-1}{2}$$

$$(2) \quad x = \frac{y^2}{4}$$

$$(3) \quad \frac{y}{2} = x^3 - \frac{1}{2}$$

السؤال الأول: ارسم الدوال الآتية

$$(4) \quad 2y = 4 - 3x$$

(١٠) درجة

$$x \sin y = (y \cos 2x - 3y^2)$$

(١٠) درجة

$$\int 4 \sec^2 3x \tan 3x \, dx$$

السؤال الثاني:

$$(أ) \quad \text{جد } \frac{dy}{dx} \text{ للدالة التالية}$$

(ب) جد ناتج التكامل التالي

(٢٠) درجة

$$A = \begin{bmatrix} -3 & 0.3 \\ 0.5 & 2.6 \\ -0.7 & 1 \end{bmatrix} \quad B = \begin{bmatrix} 7 & -0.9 & 0 \\ -1 & 8 & 1.9 \end{bmatrix}$$

السؤال الثالث: اذا كان

A.B ج حاصل ضرب

(٢٠) درجة

$$(1) \int \left(3x - \frac{5}{2}x^2\right) (3 - 5x) \, dx$$

$$(2) \int \sin^3 x \, dx$$

السؤال الرابع: جد ناتج التكاملات التالية

(٢٠) درجة


السؤال الخامس: جد معكوس المصفوفة :

$$\begin{bmatrix} 3 & -1 & 0 \\ -1 & 8 & 12 \\ 9 & 0 & 13 \end{bmatrix}$$

((تمىياتنا لطلبنا الأعزاء بال توفيق والنجاح))

رئيس القسم
م.م. كرلا سالم عباس

مدرس الماده
مهند نعمة عبد السيد

 

Q4/Listen and completes the questions.

- 1- Do you live?
- 2- are you married to?
- 3- does your husband do?
- 4- are you in Sydney again?
- 5- are the kids in the photos?
- 6- old are they
- 7- do your daughters have Swedish names? Because
- 8- shows do you do every year?
- 9- do you work so hard?
- 10-.....do you do in your free time?

(20 Marks)

Q5/ Listen and complete the sentences.

- 1-He gets up at And he has a shower.
- 2- He has breakfast at
- 3- He leaves home at and he goes to work by taxi .
- 4-He has lunch(a Coca-cola and a sandwich) in his office at
- 5-He always works late. He leaves work at in the evening.
- 6-He sometimes buys a pizza and eats it at home. He gets home at
- 7-He never goes out in the evening. He works at his computer until.....
- 8-He always goes to bed at.....

(16 Marks)

Q6/listen and write the words.

(14 Marks)

BEST OF LUCK




Examiner

Safa Y. Mohammed



Head of department

Karar S. Abbas

 




Final Exam 2018/2019 - Model no. (3)

Q1/ (Answer two only): (20 Mark)

- A: Write the logic and ladder program to implement positive and negative triggered JK flip-flop.
B: Design the logic and ladder program to implement full adder function.
C: Write the logic and ladder program to implement RS flip-flop.

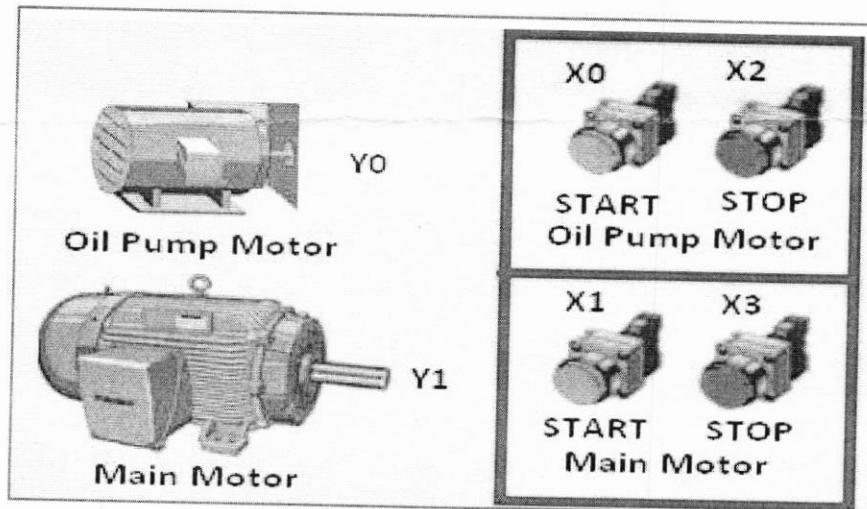Q2/ (20 Mark)


- A: Write the PLC ladder program for Providing lubricant for the gear box before the lathe spindle starts to run which aims to ensure that the oil pump motor starts first and the main motor starts subsequently.



- B: Write the PLC ladder program for (ON and OFF) delay Motor starter.

 
Q3/ (20 Mark)

- A: Write the PLC ladder program to implement an Automatic liquid mixing machine.
B: Write the PLC ladder program to implement a three-phase induction motor bidirectional delta/ star starter (using TON).



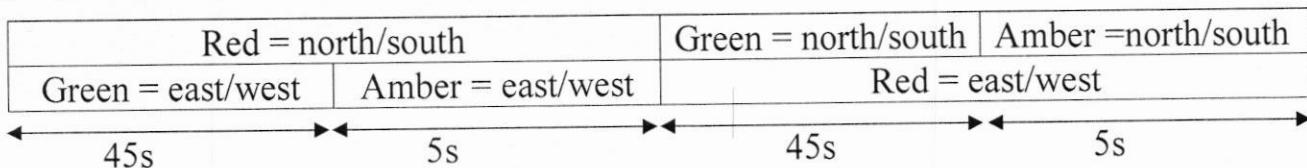Q4/ (20 Mark)

A: The time chart for two direction control traffic lights is shown below, write a PLC ladder program to achieve that. Use any type of timer instructions.




B: Draw the PLC based solution for the following function:

$$F = A \cdot \bar{B} \cdot D + \bar{C} \cdot D \cdot A + B \cdot C$$

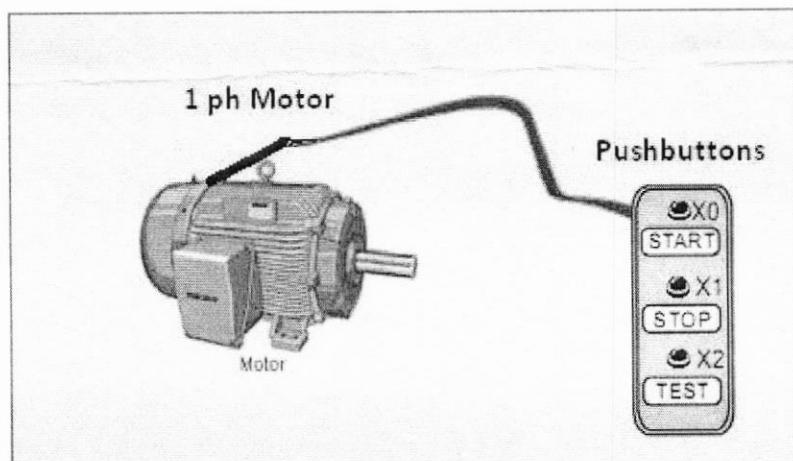Q5/ (20 Mark)

A: Write the PLC ladder program for controlling the running state of the 1 ph motor by pressing START and STOP pushbuttons, motor should remain in ON state after START pushbutton is pressed and should OFF when STOP pushbutton is pressed. Checking if the Motor is running normally by pressing TEST pushbutton.



B: Write the logic and ladder program to implement an exclusive OR gate function.

BEST OF LUCK

saif m.r


Lecturer

Saif Muneam Ramadham

Karar Salim Abbas

Head of department

Karar Salim Abbas

 



اسئلة الامتحان النهائي للعام الدراسي 2018/2019 نموذج رقم (١) الدور الثالث

ملاحظة: أجب عن جميع الأسئلة (كل سؤال 20 درجة/لكل فرع 10 درجات)

س¹/ اجب عن فرعين فقط:

- أ) عدد بالتفصيل أجزاء ماكينة التيار المستمر مع ذكر وضيفة كل جزء منها.
 ب)وضح مبدأ عمل مولدات التيار المستمر.
 ج) مولدان تيار مستمر من النوع التوازي متماثلان يعملان على التوازي ليجهزا حمل كلي بتيار (A 4000). إذا كانت ق.د.ك. للمولد الأول (V 490) وللمولد الثاني (V 480). احسب القدرة المجهزة من كل مولد إذا علمت أن مقاومة المنتج (Ω) و مقاومة المجال (Ω) لكل منها.

س²

- أ) ما هو بادئ الحركة (Starter) في محركات التيار المستمر؟ وما الغرض من استخدامه؟ واشرح مع الرسم عمل بادئ الحركة اليدوي.
 ب) محرك تيار مستمر من النوع التوازي يغذي حمل قدرته (HP 150) عند الحمل الكامل ويدور بسرعة (16 r.p.s.) موصول إلى مصدر جهد (V 550). فإذا كانت كفاءة المحرك (%) 91% و مقاومة ملفات التوازي (Ω) 275 و مقاومة المنتج (Ω) احسب المفروقات الحديدية والميكانيكية وعزم الدوران عند الحمل الكامل.

س³

- أ) صنف المحولات الكهربائية بحسب تطبيقاتها واذكر استخدام كل نوع منها.
 ب) محول احادي الطور قدرته (0.1MVA) ونسبة التحويل (4/20) يملك عناصر الدائرة المكافئة التالية ($X_2=0.75 \Omega$, $X_1=0.035 \Omega$, $R_1=0.015 \Omega$, $R_2=0.25 \Omega$, $R_0=500 \Omega$, $X_0= 150 \Omega$) ويغذي حمل بقدرة (0.09MVA) عند جهد (2000V) و معامل قدرة (0.8lag) متاخر احسب معامل القدرة للفل الابتدائي.

س⁴

- أ) كيف يمكن حساب R_2 , X_m , R_1 , X_1 في المحرك الحشبي الأحادي الطور؟
 ب) محرك حشبي ثلاثي الطور ذو اربع خطوط يغذى من مصدر بتردد 50Hz احسب:
 I. السرعة التزامنية.
 II. تردد الجزء الدوار عند معامل انزلاق 0.04
 III. سرعة الدوران عند اللاحم.
 IV. تردد الجزء الدوار عند بدء الحركة.


س⁵

- أ) وضح مع الرسم عملية ربط المولدات التزامنية على التوازي باستخدام جهاز التزامن.
- ب) مولد تزامني ثلاثي الاطوار له 16 قطب يجهز حمل بقدرة (10MVA) ويدور بسرعة (375r.p.m.) اذا علمت ان معامل اللف هو (0.96) والفيض المغناطيسي يساوي (0.03Wb) كم موصل يحتاج المولد ليعطي ق.د.ك. مقدارها .(2.655kV)


((تمنياتنا لطلبتنا الأعزاء بالتوفيق والنجاح))



رئيس القسم
م.م. كرار سالم عباس

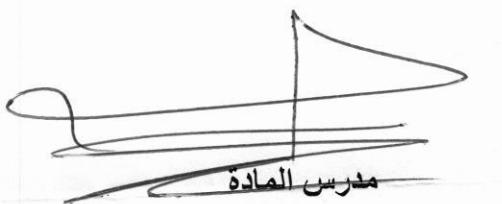

 مدرس المادة
م.م. زين الدين سعيد عبد الرحمن





المادة: تطبيقات الحاسوب
الصف: الاول / صباحي
الزمن: ثالث ساعات
التاريخ: ١١ / ٢ / ٢٠١٩

اسئلة الامتحان النهائي للعام الدراسي 2018/2019 نموذج رقم (3) الدور الثلث

ملاحظة: أجب عن جميع الاسئلة

السؤال الأول: اجب عن فرعين

أ/ ما هي خيارات الامر trim ؟

ب/ ما هي مكونات واجهة برنامج AutoCAD ؟

ج/ ما هي اسباب ظهور كلمة offset مفردة في صيغة الجمع في اوامر اخرى ؟

السؤال الثاني: أ/ في برنامج AutoCAD طريقة الكتابة بأمر text ما هما ؟

ب/ عرف ما يأتي:-

Array -2 Mirror -1

ج/ كيف يتم الاستفادة من أمر explode التفجير ؟

السؤال الثالث: اجب عن فرعين

أ/ ما هي عدادات الوصول الى حسابات المستخدمين في الحاسوب ؟

ب/ تكلم عن استنساخ ونقل ملف بالتفصيل ؟


ج/ عرف الادوات الذكية وكيف يتم احضارها داخل الحاسوب بالتفصيل ؟

السؤال الرابع: أ/ وضح عملية معالجة البيانات باستخدام وحدة المعالجة المركزية؟ من خلال المخطط فقط.

ب/ ما هي خصائص الحاسوب ؟

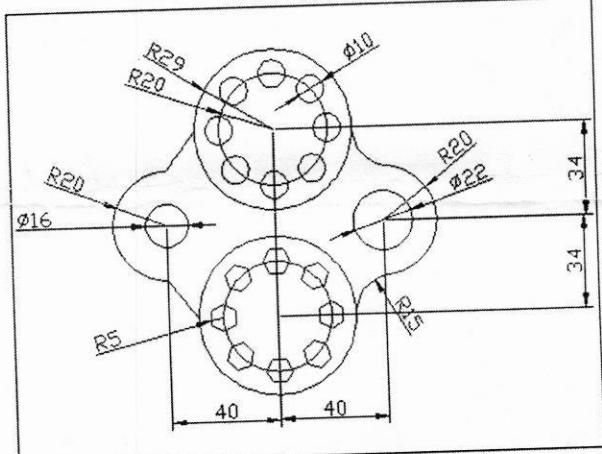(10) درجة


السؤال الخامس: أ/ اكتب خطوات الرسم التالي بالتفصيل :





السؤال الخامس: بـ / اكتب خطوات الرسم التالي بالتفصيل :

(10) درجة

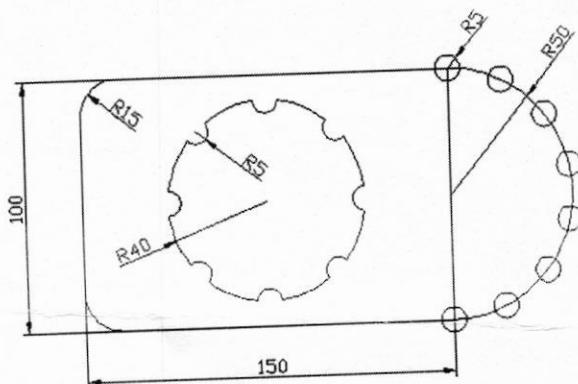

((تمنياتنا لطلبتنا الأعزاء بالتوفيق والنجاح))

م.م. كرار سالم عباس
رئيس القسم

مدرس الملاحة
نور صادق احمد



Ministry of Higher Education &
Scientific Research
Southern Technical University
Technical Institute / Qurna
Dep. of Electrical Techniques



Subject: power electronics
Class: Second – Morning
Time: Three Hours
Date: ٤ / ١١ / ٢٠١٩

Final Exam 2018/2019 - Model no. (2)-(3) Attempt

Note: Answer All Question

Q1/Answer only one

$$V_{dc} = \frac{3 V_m}{\sqrt{3}}$$

$$V_m = 500$$

(12.5 Mark)


A- 3-Phase Bridge rectifier with $\Delta - Y$ transformer and (250W, 10Ω) resistive load. Plot circuit diagram, then Find the value of the secondary line voltage.

B-3-Phase half -wave rectifier with delta-star transformer is connected to 10 Ω resistive load. For 220 V secondary line to line voltage and 50 Hz. Calculate

- 1- The dc load power
- 2- the conduction time of each diode.

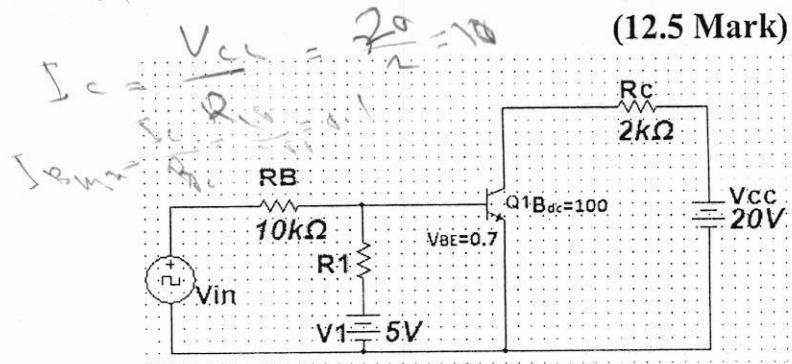Q2/ For the following circuit Find

- 1- The value of R1
- 2- The value of Vin



(12.5 Mark)

Q3/ A UJT (UNJUNCTIONAL TRANSISTOR) has the following data: $V_{BB}=30V$, $R_1=100K\Omega$, $V_D= 0.6V$, $\eta = 0.65$.

- 1- What is the value of C_1 that gives 1KHz output frequency.
- 2- Calculate the maximum value of the capacitor voltage.

(12.5 Mark)

Q4/ For OP-AMP Signal Generation, fill the blank in the following in the table. (12.5 Mark)

No.	Resistances	V_{cc}	R_f	C	K	V_b	Frequency (F)
1.	$R_a = R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_1 =$	$V_{b1} =$	$F_1 =$
2.	$R_a = 2R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_2 =$	$V_{b2} =$	$F_2 =$
3.	$R_a = 3R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_3 =$	$V_{b3} =$	$F_3 =$

$$V_b = \frac{R_b}{R_2 + R_b} V_{cc}$$

Flip the paper

$$F = \frac{1}{T_1}, T_1 = 2R_f C \ln \frac{1+K}{1-K}$$

$$I_{B3} = \frac{V_{in} - V_{BE}}{R_B}$$

9565

Q5/ Answer the following

(12.5 Mark)

- A- what are the different methods to turn on the thyristor?
- B- what are the disadvantage of an SCR over mechanical switch?
- C- Discuss the different between the diode and thyristor in details?
- D- Represent the SUS thyristor by using 1) two transistor 2) three diode?

Q6/3-Phase half controlled rectifier is used to controlled [3240w] power of 10Ω dc load, for 400v line to line voltage. 1- Plot circuit diagram 2- Find the value of firing angle $[\alpha]$

(12.5 Mark)

$$V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

Q7/ Answer only one

(12.5 Mark)

- A- Design parallel invertor of maximum frequency ($F_{max} = 400\text{Hz}$) and supply ac load (120-watt, 240 volt) using 12-volt battery, $t_{on} = 3 \times t_{off}$

- B- thyristor step up chopper has the following data: - $V_s = 50\text{v}$, chopping frequency = 250Hz, $T_{off} = 2\text{msec}$ Calculate V_o

Q8 Thyristor AC Controllers with 7Ω resistive load is connected to ac voltage source $v_{in} = 350\sin 315t$, if the conduction time of each thyristor is (2.5msec), calculate the load power.

(12.5 Mark)

BEST OF LUCK

Lecturer

Abdulghafar Abdulghafar Abdulhameed

Head of department

Karar Salim Abbas

$$V_{dc} = \frac{P_{dc}}{R} =$$

$$P_{dc} = \frac{V^2}{R}$$

39400




Final Exam 2018/2019 - Model no. (١) - (٣) Attempt

Note: Answer All Questions

Q1/ A) Find the input impedance Z_{in} if $\omega = 50 \text{ rad/sec}$?


(15 Mark)

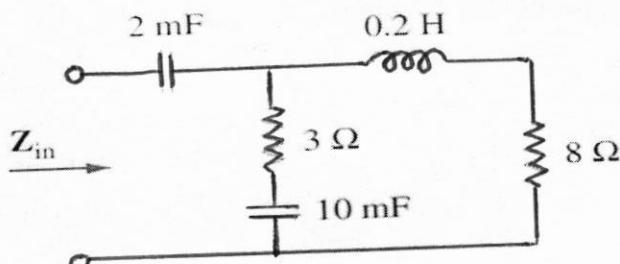

Q1/ B) Determine the energy expended moving a charge of $50 \mu\text{C}$ through a potential difference of 6 V . (5 Mark)

Q1/ C) The charge flowing through the imaginary surface is 0.16 C every 64 ms . Determine the current in amperes? (5 Mark)

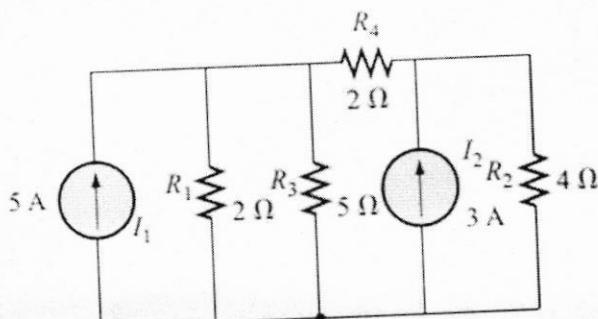
Q2/ Find the current through 4Ω resistor using mesh analysis? (25 Mark)




Q3/Choose two:

A) Given $i_1(t) = 4 \cos(\omega t + 30^\circ)$ and $i_2(t) = 5 \sin(\omega t - 20^\circ)$ find their sum ? (12.5 Mark)

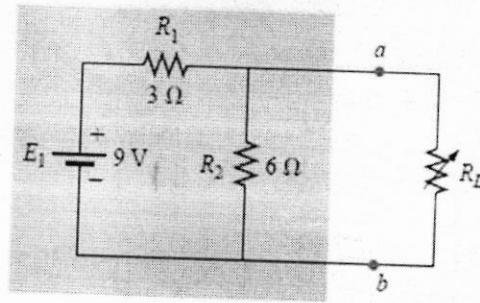
B) Find the Thévenin equivalent circuit for the shaded area. Then find the current through R_L for values of $(2, 10, \text{and } 100 \Omega)$? (12.5 Mark)



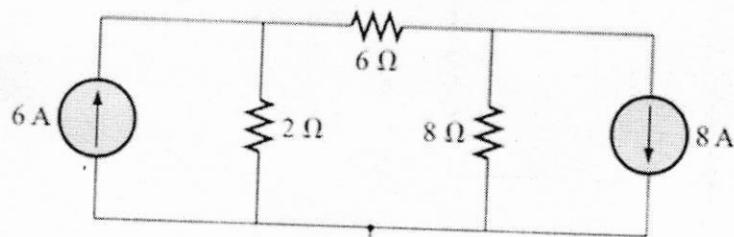C) Find the current through $6\text{-}\Omega$ resistor using superposition theorem? (12.5 Mark)



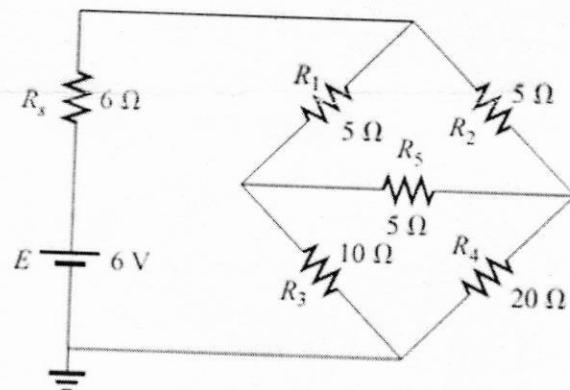Q4/ Find voltage across $6\text{-}\Omega$ resistor in the circuit below ? (25 Mark)



BEST WISHES

Lecturer
Karrar Salim Abass

Head of department
Karrar Salim Abass



Final Exam 2018/2019 - Model no. (2)-(3) Attempt

Note: Answer All Question

(12.5 Mark)


Q1/Answer only one

A- 3-Phase Bridge rectifier with $\Delta - Y$ transformer and (250W, 10Ω) resistive load. Plot circuit diagram, then Find the value of the secondary line voltage.

B-3-Phase half-wave rectifier with delta-star transformer is connected to 10 Ω resistive load. For 220 V secondary line to line voltage and 50 Hz. Calculate
1- The dc load power 2- the conduction time of each diode.

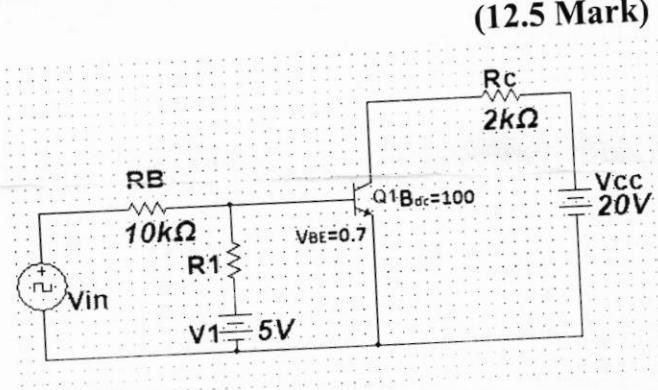Q2/ For the following circuit Find

- 1- The value of R_1
- 2- The value of V_{in}



Q3/ A UJT (UNJUNCTIONAL TRANSISTOR) has the following data: $V_{BB}=30V$, $R_1=100K\Omega$, $V_D= 0.6V$, $\eta = 0.65$.

- 1- What is the value of C_1 that gives 1KHz output frequency.
- 2- Calculate the maximum value of the capacitor voltage.


(12.5 Mark)

Q4/ For OP-AMP Signal Generation, fill the blank in the following in the table.

(12.5 Mark)

No.	Resistances	V_{cc}	R_f	C	K	V_b	Frequency (F)
1.	$R_a = R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_1 =$	$V_{b1} =$	$F_1 =$
2.	$R_a = 2R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_2 =$	$V_{b2} =$	$F_2 =$
3.	$R_a = 3R_b$	± 18	$10K\Omega$	$0.1\mu F$	$K_3 =$	$V_{b3} =$	$F_3 =$

Flip the paper

 

Q5/ Answer the following

(12.5 Mark)

A- what are the different methods to turn on the thyristor?

B- what are the disadvantage of an SCR over mechanical switch?

C- Discuss the different between the diode and thyristor in details?

D- Represent the SUS thyristor by using 1) two transistor 2) three diode?

Q6/ 3-Phase half controlled rectifier is used to controlled [3240w] power of 10Ω dc load, for 400v line to line voltage. 1- Plot circuit diagram 2- Find the value of firing angle $[\alpha]$

(12.5 Mark)

Q7/ Answer only one

(12.5 Mark)


A- Design parallel invertor of maximum frequency ($F_{max} = 400Hz$) and supply ac load (120-watt, 240 volt) using 12-volt battery, $t_{on} = 3 \times t_{off}$

B- thyristor step up chopper has the following data: - $V_s = 50v$, chopping frequency = 250Hz, $T_{off} = 2msec$ Calculate V_o

Q8 Thyristor AC Controllers with 7Ω resistive load is connected to ac voltage source $v_{in} = 350\sin 315t$, if the conduction time of each thyristor is (2.5msec), calculate the load power.

(12.5 Mark)

BEST OF LUCK

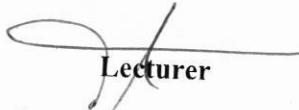

Lecturer

Abdulghafar Abdulghafar Abdulhameed



Head of department

Karar Salim Abbas

